

Introduction to Power Electronics

What is Power Electronics?

■ Power + Electronics

- Power conversion by processing electric power to expected voltage, current and / or frequency with semiconductor devices
- High frequency **>20kHz**
- Rapidly developed since 80s
- Applications
 - Industrial, commercial and residential purposes
 - Electrical vehicles, aerospace and space technologies



Applications of Power Electronics

■ Switched Mode Power Supplies (SMPS)

- Steady and regulated output voltage / current

■ Applications of SMPS


- Low voltage high current DC power supplies
- Battery chargers
- Welding machines with over 100A
- Aerospace power systems
- Several KV power supplies for radar systems, cathode ray



Applications of Power Electronics

■ Switched Mode Power Supplies (SMPS)

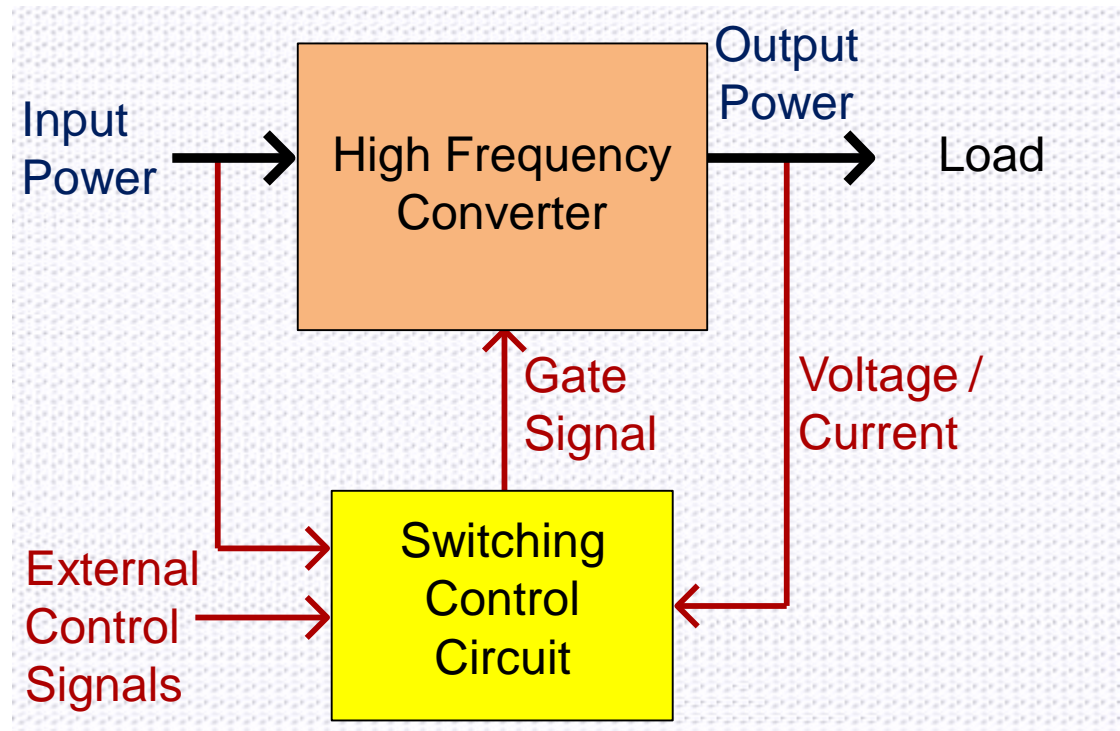- Closed loop control for regulating output
- Pulse-width-modulation (PWM), frequency modulation or phase modulation control
- Control ICs (Unitrode, Maxim)
- Microprocessors
- DSPs
- Range of operation concerned



Applications of Power Electronics

■ Inverters

- AC current or mainly voltage output
- DC/AC converters or inverters
- DC input



■ Applications of Inverters

- AC power supplies
- AC drives
- Induction heating
- Electronic ballasts

Applications of Power Electronics

- **Waveform Shaping & EMI Control Systems**
 - Shaping input / output and voltage / current
- **Applications of Waveform Shaping**
 - Switched-mode amplifiers
 - Harmonic waveform generation system
- **Applications of EMI Control**
 - Power factor correction rectifiers
 - Active filters



Applications of Power Electronics

■ Uninterruptible Power Supplies

- With DC/DC converter of charging and discharging battery
- With Inverter for AC output




■ Motor Drives

- Choppers for brush-type DC motors
- Variable speed drives (VSD) for induction motors
- Converters for brushless DC motors
- Converters for switched reluctance motors

Power Components

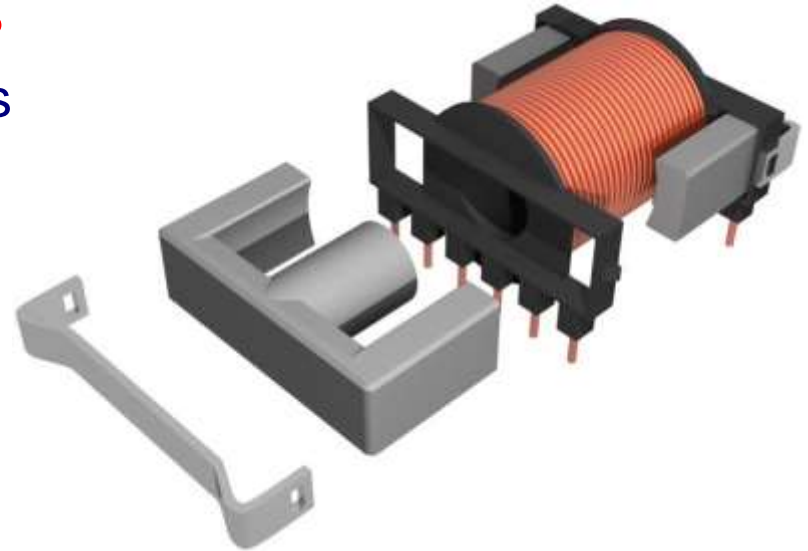- **Energy Storage Components**
 - Inductors, capacitors, transformers
- **Active Switching Devices**
 - MOSFET, IGBT
 - Thyristors (SCR),
 - Gate turn-off thyristors (GTO)
 - Bipolar Junction Transistors (BJT)
- **Passive Switching Devices**
(Power Diodes)
 - General purpose diodes
 - Ultra-fast recovery diodes
 - Schottky barrier diodes




Why high frequency?

- Small size and light weight
- Inductors

$$P_L = E_L f_s = \frac{1}{2} L I_L^2 f_s$$


- Capacitors
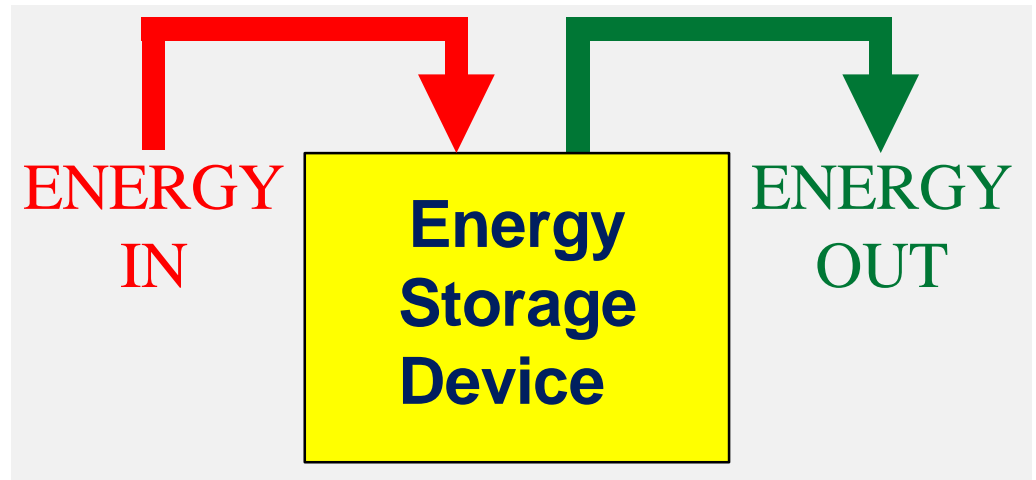
$$P_C = E_C f_s = \frac{1}{2} C V_C^2 f_s$$




Characteristics of Active Switching Devices


■ Symbol of Active Switching Devices

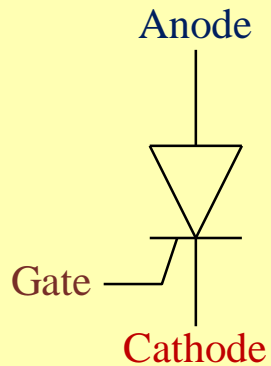


Thyristor

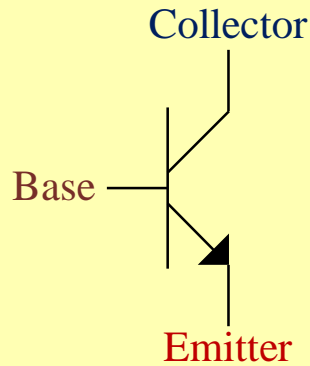


BJT

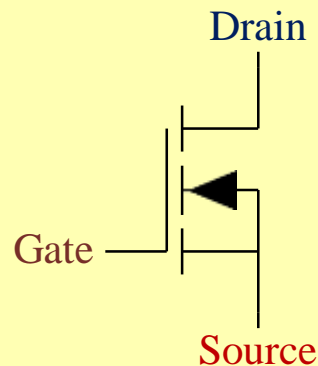

MOSFET

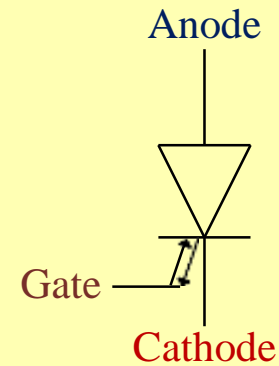

GTO

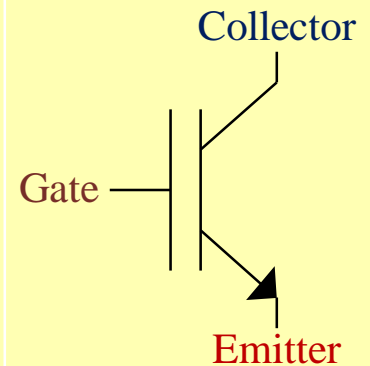

IGBT

Characteristics of Active Switching Devices


- **Thyristor / Silicon Controlled Rectifier(SCR)**
 - Developed in 1960s
 - Switched on by a short injecting gate current pulse
 - **Firing or Triggering**
 - Switched off when reverse biased
 - Ratings up to 5kV and 4000A
 - **Very high power applications**
 - Around 2V on-state voltage
 - Slow response
 - $f_S < 1\text{kHz}$
 - Force commutation necessary



Characteristics of Active Switching Devices

■ Bipolar Junction Transistor (BJT)

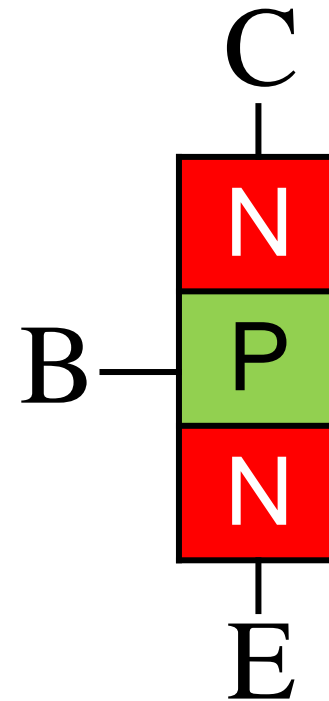- Controlled by base current
- On and off only
 - Linear region avoid
- Ratings up to 1kV and 4000A
- Very high power applications
- On-state voltage >1V
- $f_S < 5\text{kHz}$
 - Faster than thyristors
 - Slower than MOSFET and IGBT
- Rarely used



Characteristics of Active Switching Devices

■ MOSFET

- Metal Oxide Silicon Field Effect Transistor
- Developed in early 1980s
- Controlled by gate-to-source voltage (V_{gs})
 - Gate Signal, 10V to 18V, typically 15V
- Ratings up to 1000V and 2000A
 - High current low voltage applications
 - SMPS, battery chargers
- Very fast response
 - $f_s < 1\text{MHz}$, higher for soft-switching
- Bidirectional and resistive conduction characteristics



Characteristics of Active Switching Devices

- **Gate Turn-off Thyristor (GTO)**
 - Developed in mid 1980s
 - Similar to thyristor
 - Switched on by a injecting short gate current pulse
 - Switched off by reverse biased
 - Switched off by a high and short reverse current pulse
 - Ratings up to 4.5kV and 3000A
 - High power applications
 - On-state voltage 2V to 3V
 - Response faster than thyristors
 - $f_s < 2\text{kHz}$



Characteristics of Active Switching Devices


■ IGBT

- Insulated Gate Bipolar Transistor
- Developed in late 1980s
- Combination of MOSFET and BJT
- Controlled by gate-to-emitter voltage (V_{ge})
 - Same as MOSFET
- Ratings up to 3500V and 2000A
 - Medium to high power applications up to 200kW
 - Popular in Motor drives
- On-state voltage 1.7V to 3V
- Fast response
 - Typically $f_s < 40\text{kHz}$, faster for some models



Characteristics of Power Diodes

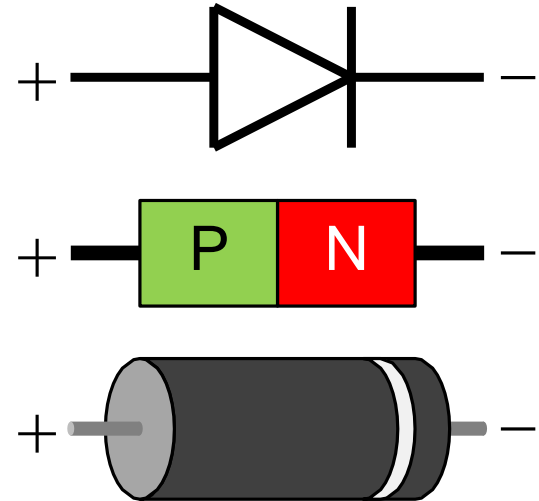
- **Comparing to Signal Diodes**
 - More complicated structure
 - Much higher V and I ratings
 - **Used in power processing**
 - Lower frequency response
 - Higher on-state voltage (forward voltage, V_F)



Characteristics of Power Diodes

■ Forward Bias

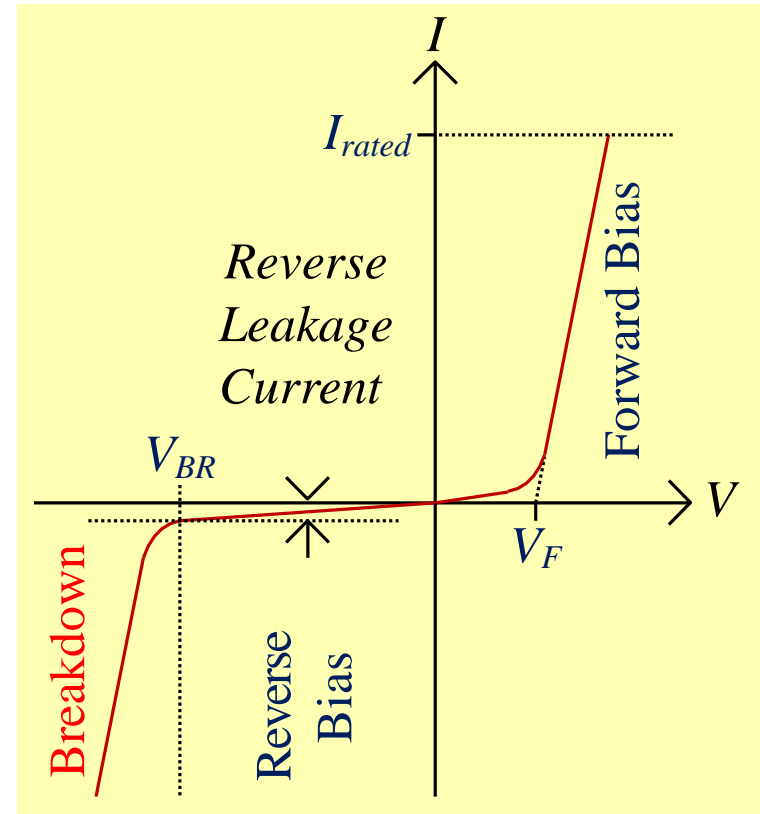- Low forward voltage drop (forward voltage, V_F)
 - Temp related
 - 0.2V to 3V
 - Decreasing with temp increase
- Typical V_F provided in datasheet




Characteristics of Power Diodes

■ Reverse Bias

□ Reverse leakage current


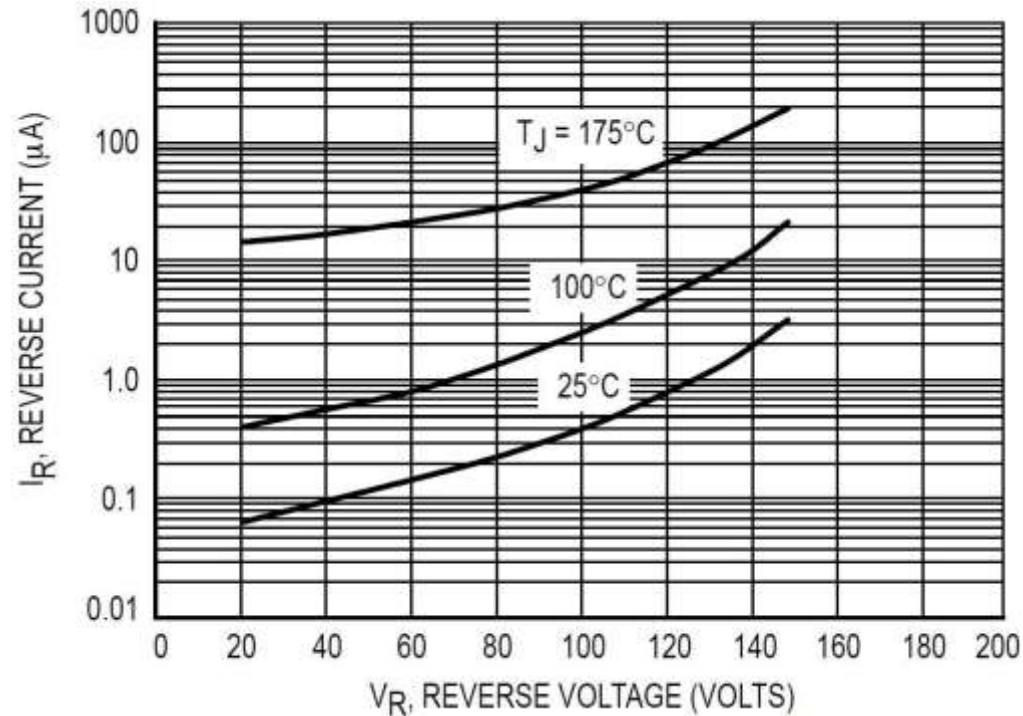
- μA to mA
- Increasing with increase of junction temp, T_j
- Increasing with increase of reverse voltage, V_R



Characteristics of Power Diodes


■ Junction Capacitance

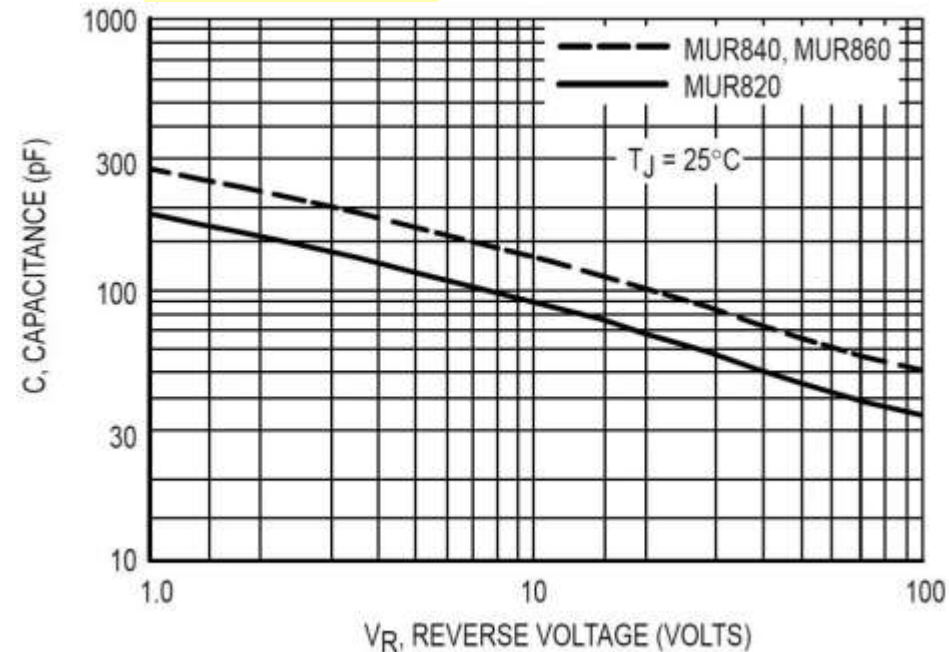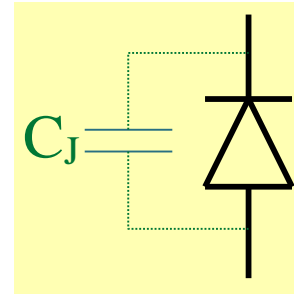- Diode as a capacitor in reverse bias
 - Junction capacitance between anode and cathode
- Parasitic oscillations caused
 - Solved by resonant converter techniques
 - Acting as resonant component
- Decreasing with the increase of reverse voltage




Forward Recovery of Power Diodes

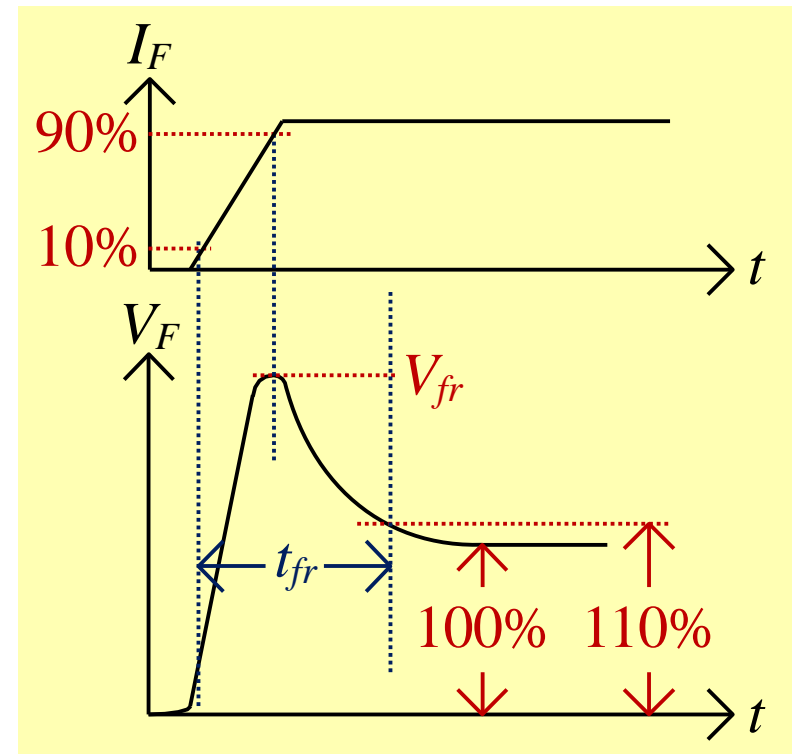- During the change from reverse bias to forward bias
- Forward voltage, V_F , increasing and back to normal
- Affecting high current and high voltage systems
- Not affecting low power systems



Reverse Recovery of Power Diodes

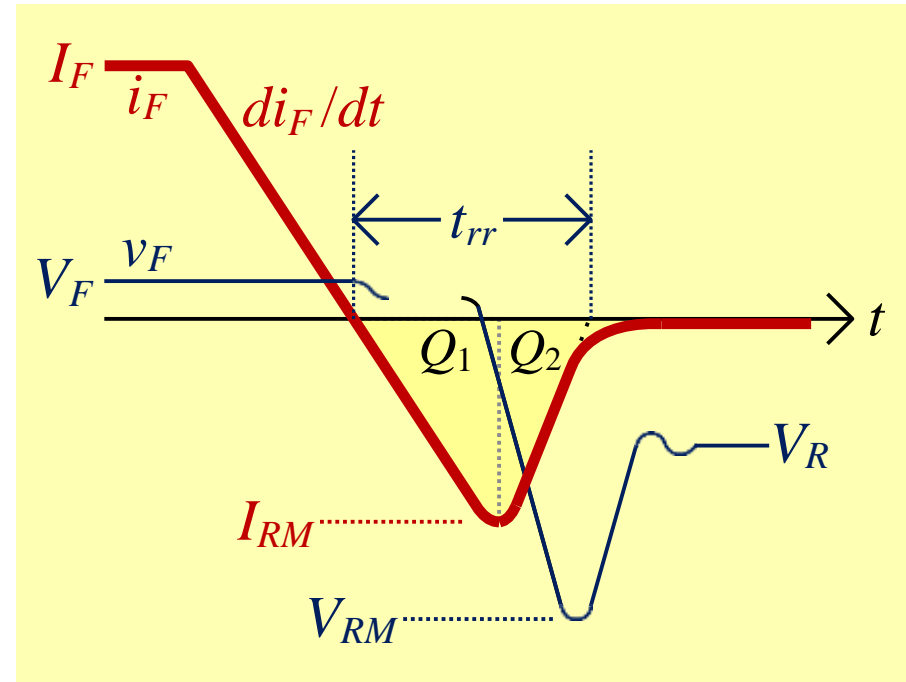- During the change from forward bias to reverse bias
- Conducting for a period
 - Minority carriers remaining in p-n junction
- Ignoring in <400Hz sine wave
- Effect significant in high frequency and square wave
- Increasing with increases of I_F and di_F/dt
- Increasing Switching losses and peak reverse voltage of diode



Types of Power Diodes


- **General Purpose Diode**
 - Highest reverse recovery
 - For low frequency applications
- **Ultra-fast Recovery Diode**
 - Very short reverse recovery period
 - Soft-recovery diodes with lower peak recovery voltage
 - High frequency and high voltage applications



Types of Power Diodes


■ Schottky Barrier Diodes

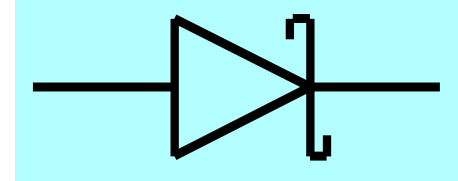- No reverse recovery
- Higher junction capacitance
- Lower voltage rating
- More expensive
- For high frequency, high performance and low voltage applications





Junction Capacitance of MOSFET / IGBT

- All devices have junction capacitance between junctions
- MOSFET / IGBT Junction Capacitors
 - Input capacitance $C_{iss} = C_{gs} + C_{gd}$
 - Gate to source
 - Charging / discharging when devices switched on / off
 - Output capacitance $C_{oss} = C_{ds} + C_{gd}$
 - Drain to source
 - Switching loss and resonance when off
 - Reverse Transfer Capacitance $C_{rss} = C_{gd}$
 - Gate to drain
 - Miller effect

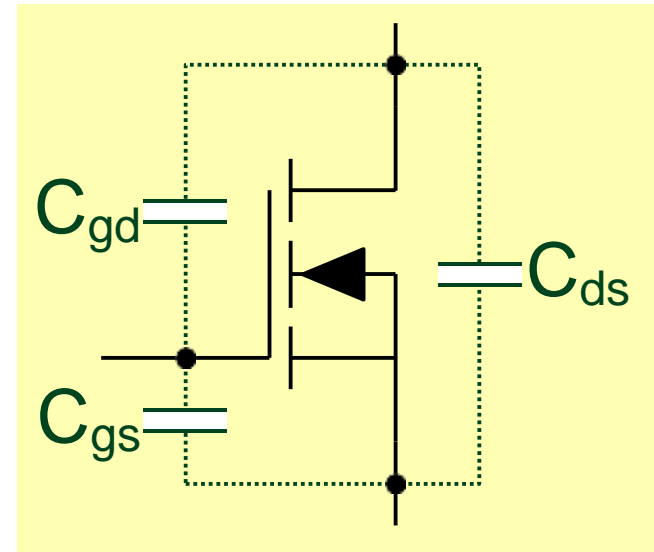


Gate Drivers for MOSFET / IGBT

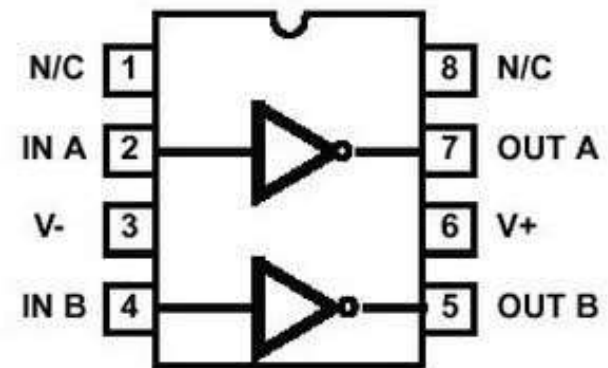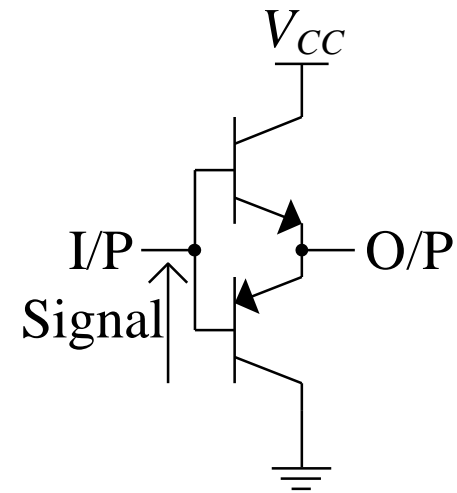- The shorter t_{on} and t_{off} , the lower conduction loss
- MOSFET / IGBT gate drivers
 - Totem-pole
 - High O/P current for charging up C_{iss} quickly
 - ICL7667, MC34151, MC34152
 - Logic-to-logic
 - High X_{in} and low X_o
 - Output $>0.4A$
 - Up to 500kHz



Non-floating Gate Drive Circuit

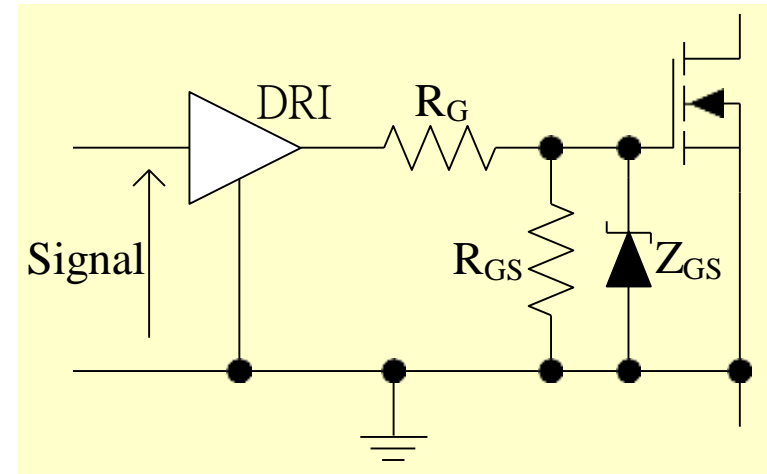- Gate / emitter connected to ground
- R_G
 - Limiting charging current of junction capacitor
 - Damping swing of v_{gs}
 - 8 to 33 Ω suggested
- R_{GS}
 - Speeding up discharging of junction capacitor
 - 1k Ω to 10k Ω
- Z_{GS}
 - Suppressing v_{gs} transient voltage
 - Voltage rating = peak output voltage of DRI



Floating Gate Drive Circuits

- Gate / emitter connected to ground
- Small pulse 1:1 transformer


- Electrical isolation

- C_1 filtering DC component of O/P of DRI


- $V_{dri}/2$ to $-V_{dri}/2$

- C_2 recovering the voltage from DC to AC square wave

- V_{dri} to 0

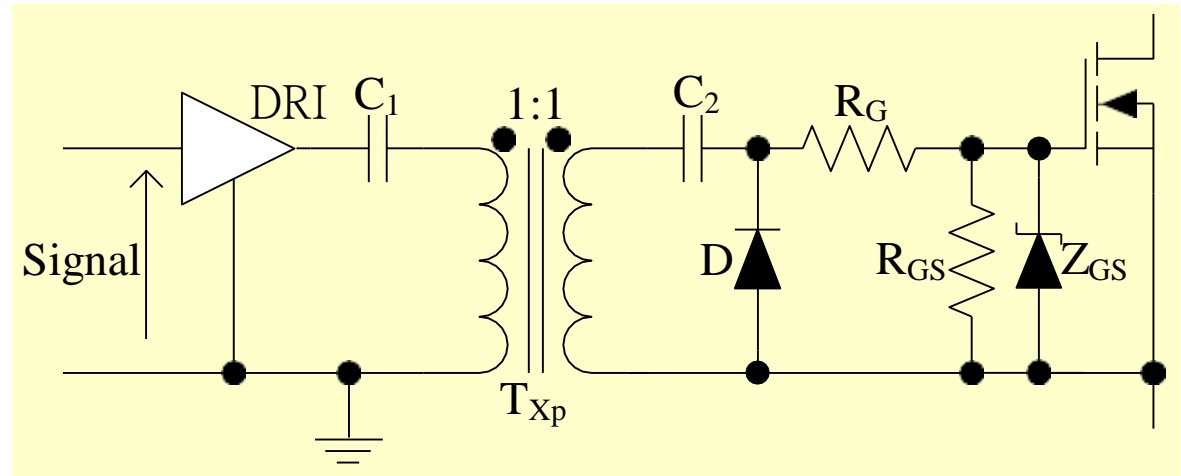

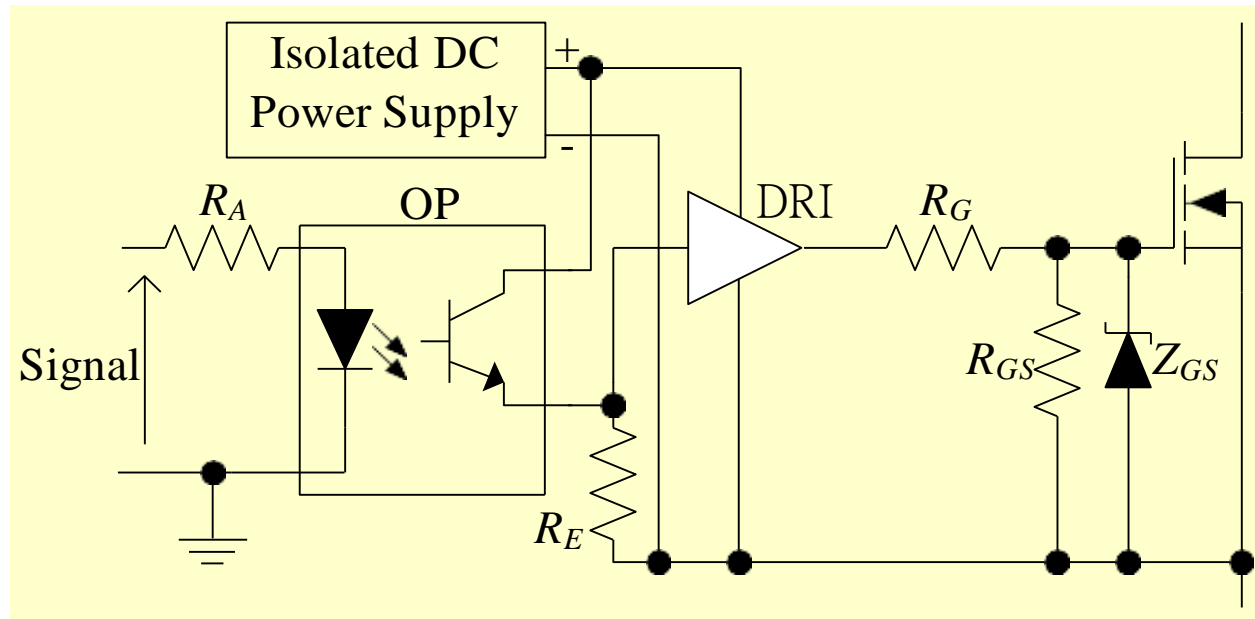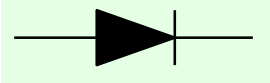
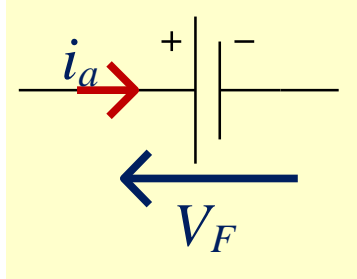

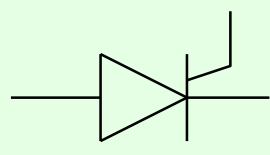
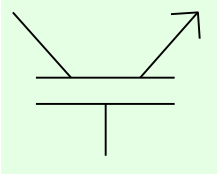
Floating Gate Drive Circuits



- **Optocoupler**
 - Electrical Isolation
- **Very low power isolated DC power supply**
 - Powering OP and DRI

Conduction Characteristic and Conduction Losses

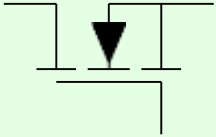

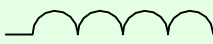
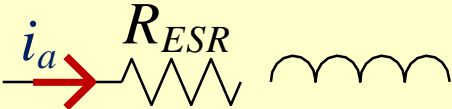
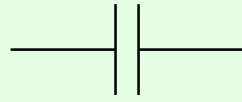

- **Forward Voltage**
 - Diodes
 - IGBTs
 - BJTs
 - Thyristors

Devices	Conduction Equivalent Circuit	Conduction Loss
 <p>Diode</p>		
 <p>Thyristor</p>		
 <p>IGBT</p>		

Conduction Characteristic and Conduction Losses



■ Resistive

- Inductors
- Capacitors
- MOSFETs

Devices	Conduction Equivalent Circuit	Conduction Loss
 MOSFET		$I_{a(rms)}^2 R_{ds}$
 Inductor		$I_{a(rms)}^2 R_{ESR}$
 Capacitor		$I_{a(rms)}^2 R_{ESR}$

Cooling Devices

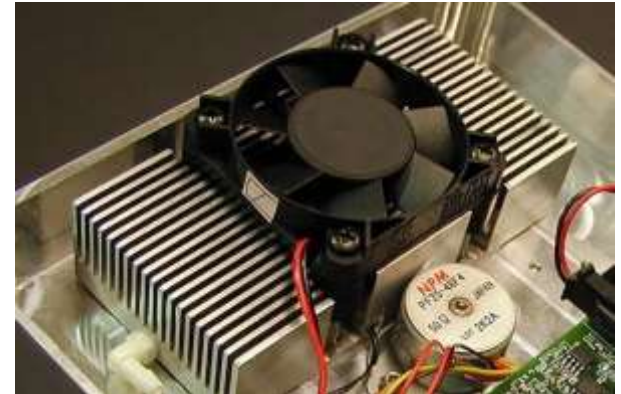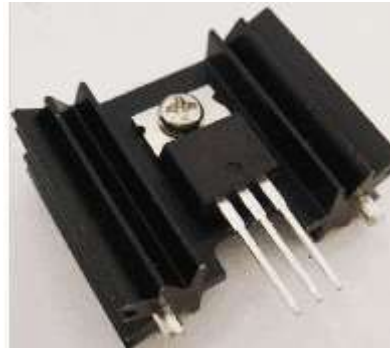
- Most power losses of devices converted into heat
 - Heat dissipation for long lifetime of devices
 - Too small surface area to flow heat to surrounding medium



Cooling Devices

■ Air convection cooling

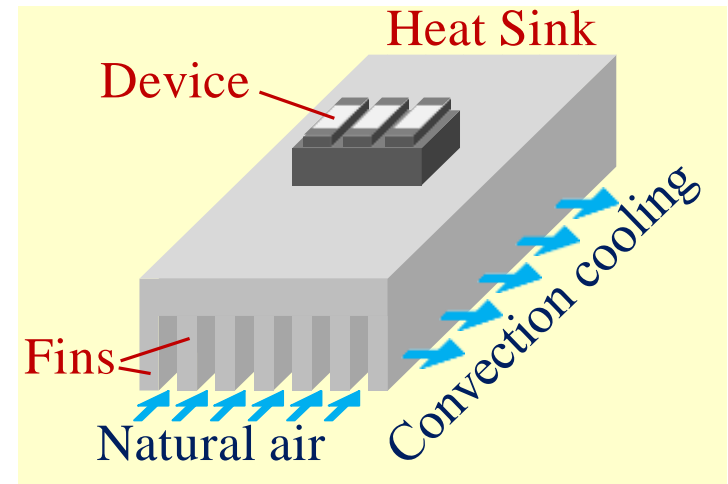- Low to medium power
- Heat sink
 - Finned aluminium
 - Increasing surface area
 - Decreasing thermal resistance
- Fan
 - Increasing air flow
- The change of temp of device



$$\Delta T = T_j - T_a = P_{loss} \left(R_{j-c} + R_{c-h} + R_{h-a} \right)$$

Reference

https://www.google.com/search?q=ppt+of+power+electronics&rlz=1C1KMZB_enIN806IN806&oq=ppt+&aqs=chrome.69i59l2j69i57j0l5.3825j0j8&sourceid=chrome&ie=UTF-8