

# Circuit Theory

- What you will use this for
  - Power management
  - Signals between subsystems
  - Possible analog data types
- How the knowledge will help you
  - Understanding power and energy requirements
  - Behavior of digital electric signals
  - Analog signal conditioning and limitations
  - Understanding associated technologies

# Circuit theory Topics

- Circuit Topology
- Voltage, Current and Power
- Kirchoff's Laws
- Circuit components
- DC circuits
- AC circuits

# Circuit Topology

- A *circuit* consists of a mesh of loops
- Represented as branches and nodes in an undirected graph.
- Circuit components reside in the branches
- Connectivity resides in the nodes
  - Nodes represent wires
  - Wires represent equipotentials

# Voltage, Current and Power (1)

- The concept of charge
  - The Coulomb [C] – the SI unit of charge
  - An electron carries  $-1.6e-19$  [C]
  - Conservation of charge
- The concept of potential
  - Attraction/repulsion of charges
  - The electric field
  - The energy of moving a charge in a field

# Voltage, Current and Power (2)

- **Voltage** is a *difference* in electric potential
  - always taken between two points.
  - Absolute voltage is a nonsensical fiction.
  - The concept of *ground* is also a (useful) fiction.
- It is a line integral of the force exerted by an electric field on a unit charge.
- Customarily represented by  $v$  or  $V$ .
- The SI unit is the Volt [V].

# Voltage, Current and Power (3)

- **Current** is a *movement* of charge.
- It is the time derivative of charge passing through a circuit branch.
- Customarily represented by  $i$  or  $I$ .
- The SI unit is the Ampere [A].

# Voltage, Current and Power (4)

- **Power** is the product of voltage by current.
- It is the time derivative of energy delivered to or extracted from a circuit branch.
- Customarily represented by  $P$  or  $W$ .
- The SI unit is the Watt [W].

# Kirchoff's Laws

- These laws add up to nothing! Yet they completely characterize circuit behavior.
- Kirchoff's Voltage Law (KVL) - The sum of voltages taken around any loop is zero.
  - The start and end points are identical; consequently there is no potential difference between them.
- Kirchoff's Current Law (KCL) – The sum of currents entering any node is zero.
  - A consequence of the law of conservation of charge.



# Circuit components

- Active vs. Passive components
  - Active ones may generate electrical power.
  - Passive ones may store but not generate power.
- Lumped vs. Distributed Constants
  - Distributed constant components account for propagation times through the circuit branches.
  - Lumped constant components ignore these propagation times. Appropriate for circuits small relative to signal wavelengths.
- Linear, time invariant (LTI) components are those with constant component values.

# Active circuit components

- Conservation of energy: active components must get their power from *somewhere!*
- From non-electrical sources
  - Batteries (chemical)
  - Dynamos (mechanical)
  - Transducers in general (light, sound, etc.)
- From other electrical sources
  - Power supplies
  - Power transformers
  - Amplifiers

# Passive lumped constants

- Classical LTI
  - Resistors are AC/DC components.
  - Inductors are AC components (DC short circuit).
  - Capacitors are AC components (DC open circuit).
- Other components
  - Rectifier diodes.
  - Three or more terminal devices, e.g. transistors.
  - Transformers.

# DC circuits

- The basic LTI component is the Resistor
  - Customarily represented by  $R$ .
  - The SI unit is the Ohm [ $\Omega$ ].
- Ohm's Law:  $V = I R$

Ohm's and Kirchoff's laws *completely* prescribe the behavior of any DC circuit comprising LTI components.


# Example: voltage divider

Assume no current is drawn at the output terminals in measuring  $V_{out}$ . Ohm's Law requires that  $V_{R1} = I_{R1} R_1$  and  $V_{R2} = I_{R2} R_2$ , which is also  $V_{out}$ . KCL says the current leaving resistor R1 must equal the current entering R2, or  $I_{R1} = I_{R2}$ , so we can write

$V_{out} = I_{R1} R_2$ . KVL says the voltage around the loop including the battery and both resistors is 0, therefore  $V_{in} = V_{R1} + V_{out}$ , or  $V_{in} = I_{R1} R_1 + I_{R1} R_2$ .

Thus,  $I_{R1} = V_{in} / (R_1 + R_2)$ , and

$$V_{out} = V_{in} R_2 / (R_1 + R_2).$$

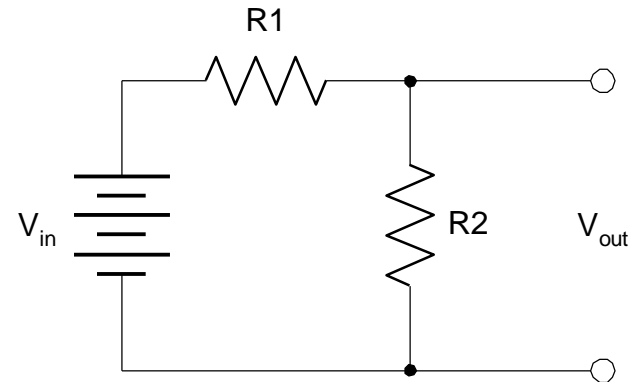

# AC circuits -- Components

- Basic LTI components
  - Resistor,  $R$ , [ $\Omega$ ] (Ohms)
  - Inductor,  $L$ , [H] (Henrys)
  - Capacitor,  $C$ , [F] (Farads)
- Frequency
  - Repetition rate,  $f$ , [Hz] (Hertz)
  - Angular,  $\omega = 2\pi f$ , [1/s] (radians/sec)

# AC Components: Inductors

- Current in an inductor generates a magnetic field,

$$B = K_1 I$$

- Changes in the field induce an inductive voltage.

$$V = K_2 (dB/dt)$$

- The instantaneous voltage is

$$V = L(dI/dt),$$

where  $L = K_1 K_2$ .

This is the time domain behavior of an inductor.

# AC Components: Capacitors

- Charge in a capacitor produces an electric field  $E$ , and thus a proportional voltage,

$$Q = C V,$$

Where  $C$  is the *capacitance*.

- The charge on the capacitor changes according to

$$I = (dQ/dt).$$

- The instantaneous current is therefore

$$I = C(dV/dt).$$

This is the time domain behavior of a capacitor.



# AC Circuits – Laplace Transform

- Transforms *differential* equations in time to *algebraic* equations in frequency ( $s$  domain).

$$F(t) \rightarrow f(s), \quad \frac{dF}{dt} \rightarrow s f(s), \quad \int F dt \rightarrow \frac{f(s)}{s},$$

where the frequency variable  $s = \sigma + j\omega$ .

For sinusoidal waves,  $\sigma = 0$ , and  $s = j\omega$ .

- Resistor behavior in  $s$  domain:  $v = iR$ .
- Inductor behavior in  $s$  domain:  $v = i(j\omega L)$ .
- Capacitor behavior in  $s$  domain:  $i = v(j\omega C)$ .


# AC circuits -- Impedance

- Impedance and Ohm's Law for AC:
  - Impedance is  $Z = R + jX$ ,  
where  $j = \sqrt{-1}$ , and  $X$  is the *reactance* in  $[\Omega]$ .
  - Ohm's AC Law in  $s$  domain:  $v = i Z$
- Resistance  $R$  dissipates power as heat.
- Reactance  $X$  stores and returns power.
  - Inductors have positive reactance  $X_l = \omega L$
  - Capacitors have negative reactance  $X_c = -1/\omega C$

# Impedance shortcuts


- The impedance of components connected in series is the complex sum of their impedances.

$$Z_s = Z_1 + Z_2 + \dots + Z_n$$

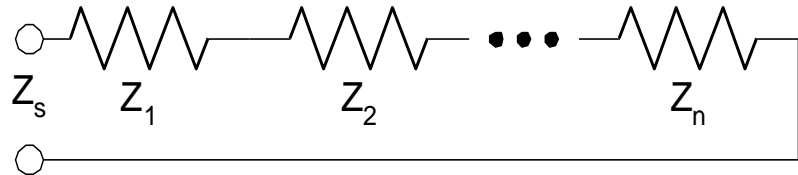

- The impedance of components connected in parallel is the reciprocal of the complex sum of their reciprocal impedances.
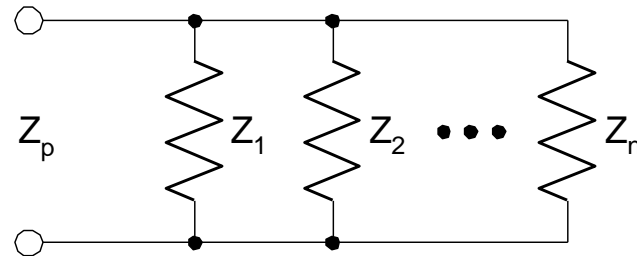
$$\frac{1}{Z_p} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_n}$$





# Example: low pass filter


Generalizing from the DC example,  $V_{out} = V_{in} \frac{Z_C}{Z_R + Z_C}$ .

Recall that  $Z_R = R$ , and  $Z_C = \frac{-j}{\omega C}$ .

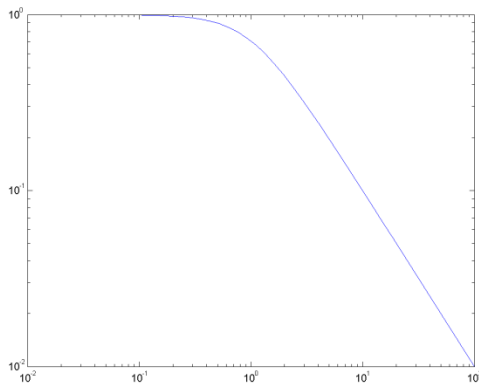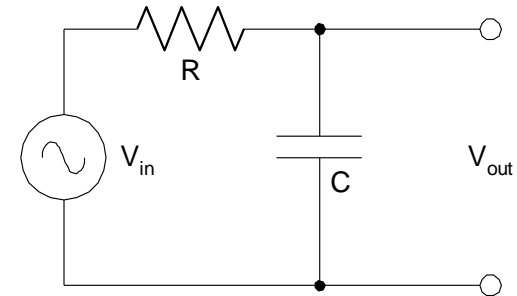
Define the filter gain  $A = \frac{V_{out}}{V_{in}} = \frac{-j/\omega C}{R - j/\omega C} = \frac{1}{1 + j\omega RC}$ .



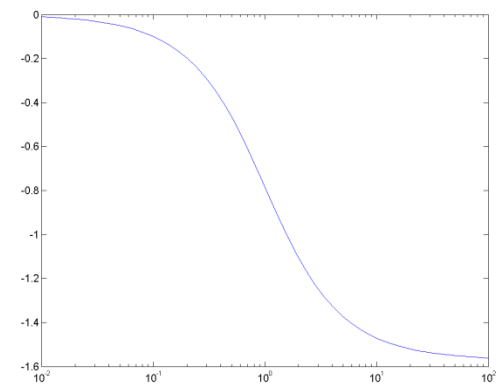Magnitude and phase plots of  $A$ , where  $RC=1$ . The magnitude plot is log/log, while the phase plot is linear radians vs. log freq.



# Homework problem

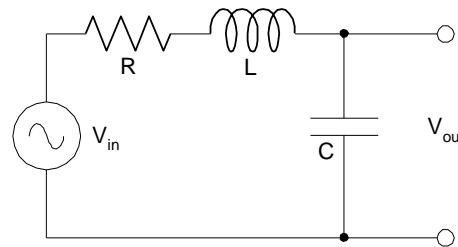

Derive the filter gain of the pictured circuit.

Plot the magnitude and phase of the filter for

$L = 6.3\text{e-}6$  [H],  $R = 16$  [ $\Omega$ ], and  $C = 1.0\text{e-}7$  [F].

For extra credit, also plot for  $R = 7$  [ $\Omega$ ] and  $50$  [ $\Omega$ ].

# Superposition Theorem

- Total current through or voltage across a resistor or branch
  - Determine by adding effects due to each source acting independently
- Replace a voltage source with a short
- Replace a current source with an open
- Find results of branches using each source independently

# Superposition Theorem

- Power
  - Not a linear quantity
  - Found by squaring voltage or current
- Theorem does not apply to power
  - To find power using superposition
  - Determine voltage or current
  - Calculate power

# Maximum power transfer Theorem

- Load should receive maximum amount of power from source
- Maximum power transfer theorem states
  - Load will receive maximum power from a circuit when resistance of the load is exactly the same as Thévenin (or Norton) equivalent resistance of the circuit



# Continued...

- To calculate maximum power delivered by source to load
  - Use  $P = V^2/R$
- Voltage across load is one half of Thévenin equivalent voltage

# References..

- NPTEL Lectures
- Sudhakarsham Mohan
- A.C Chakravarti