
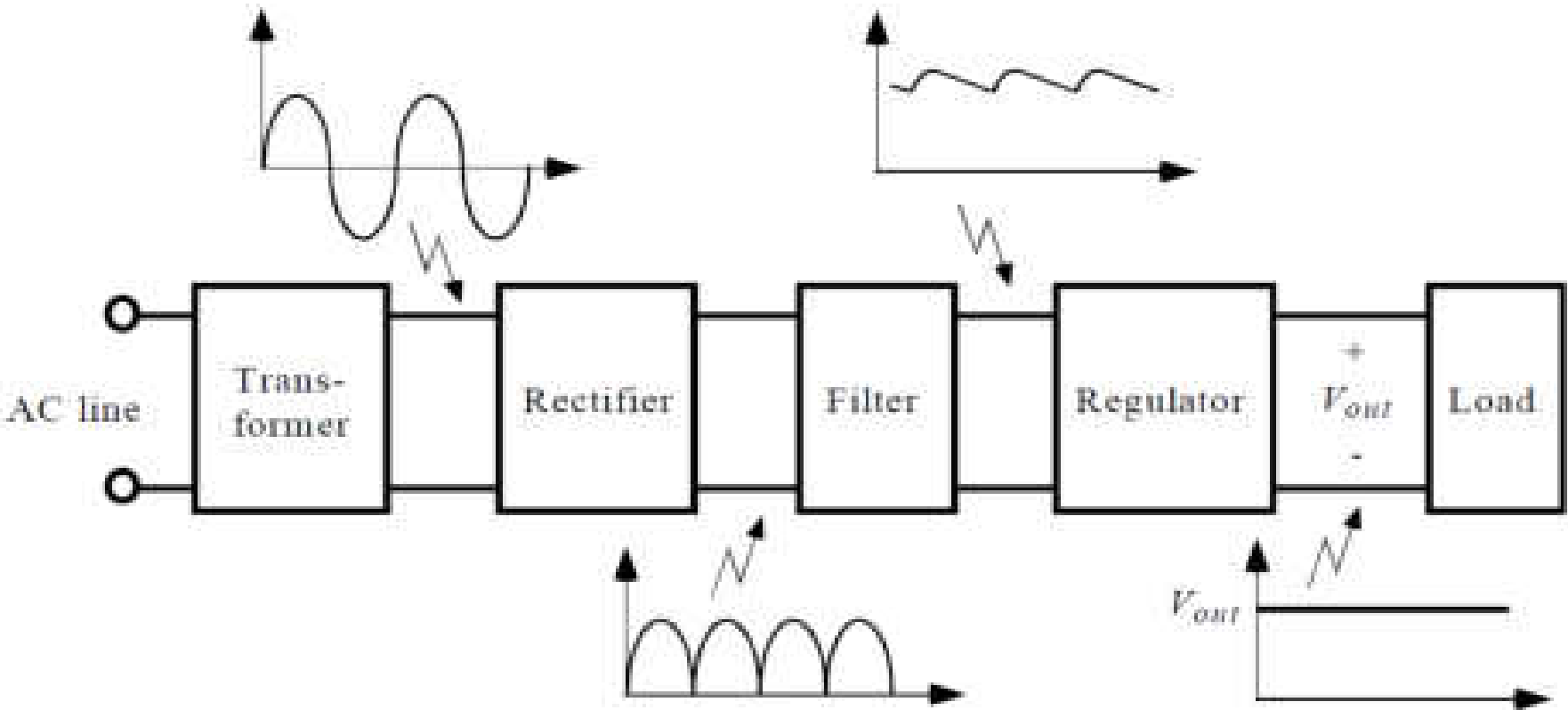


Rectifiers, Filters and Regulator Transistor Configurations and Op AMP



Dr. Supreet Singh

Basic Block Diagram of Regulated power Supply





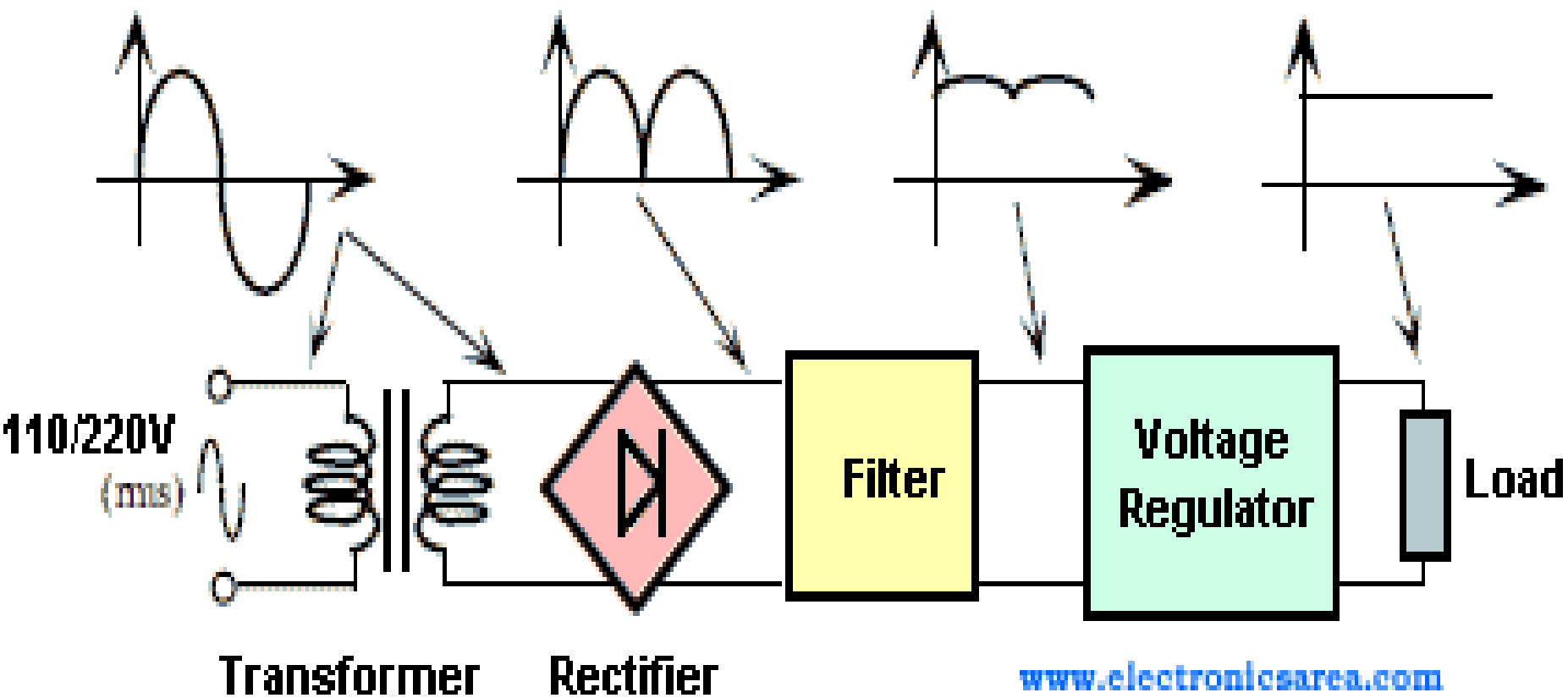




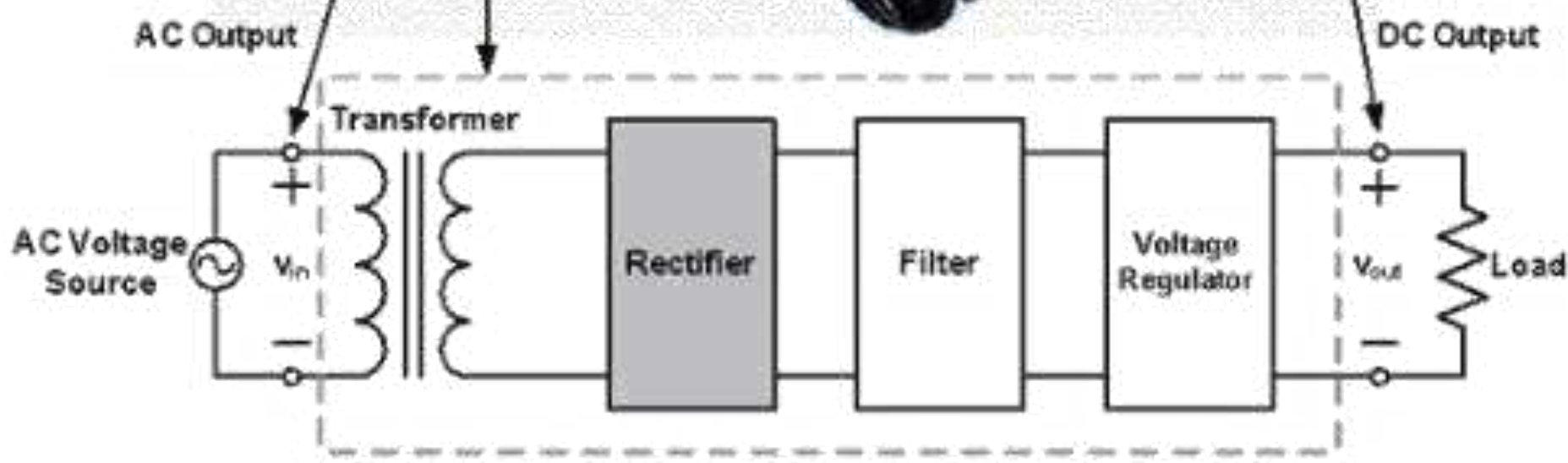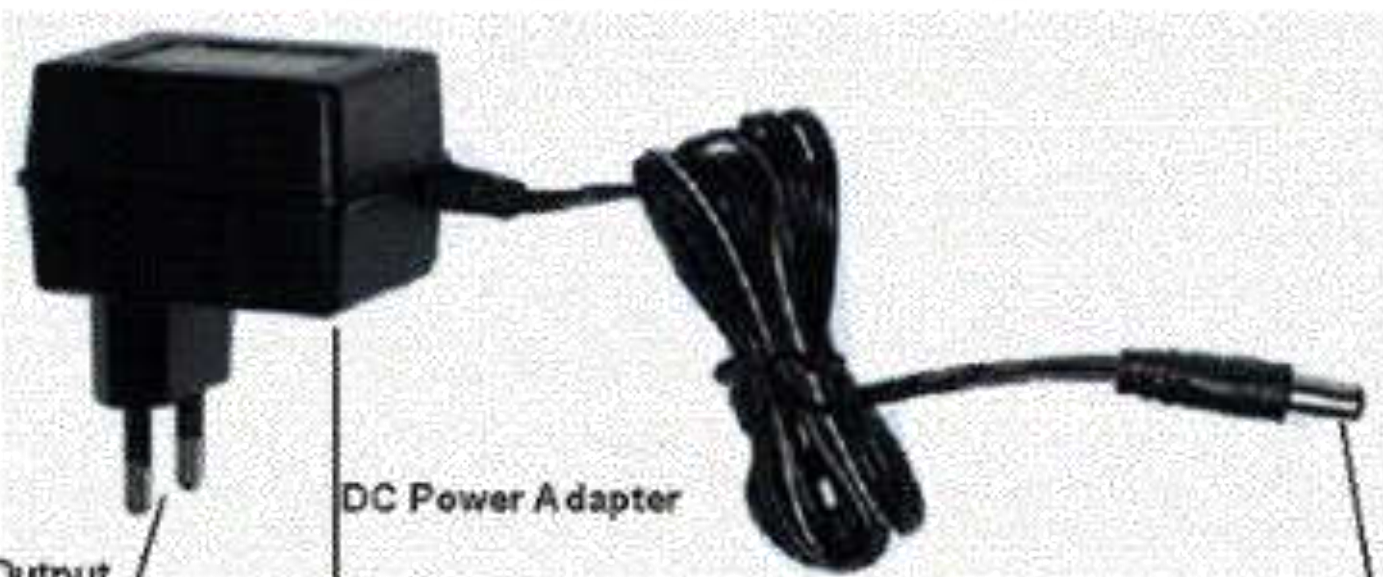Picture 1. Regulated power source Block Diagram



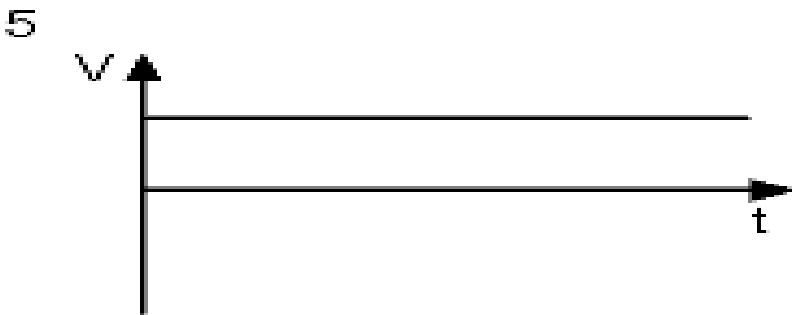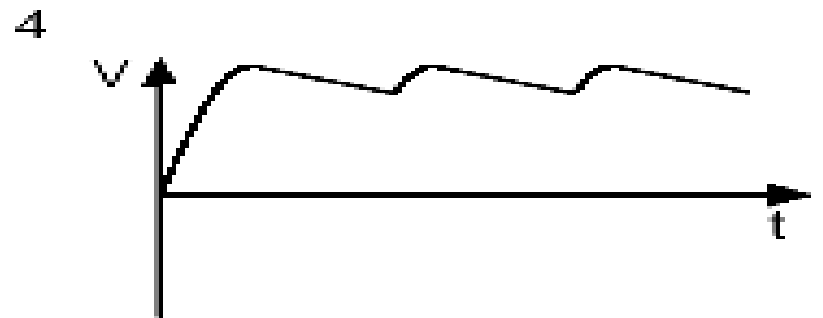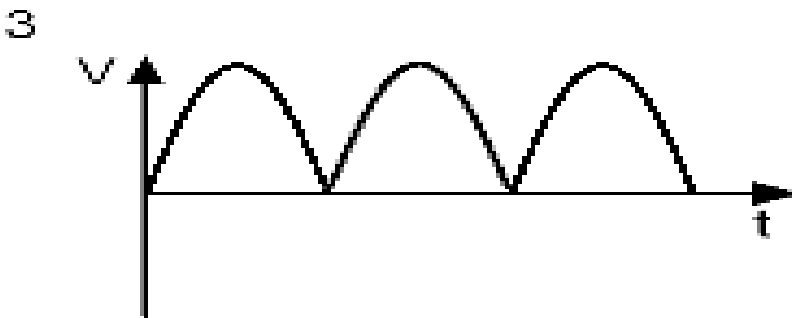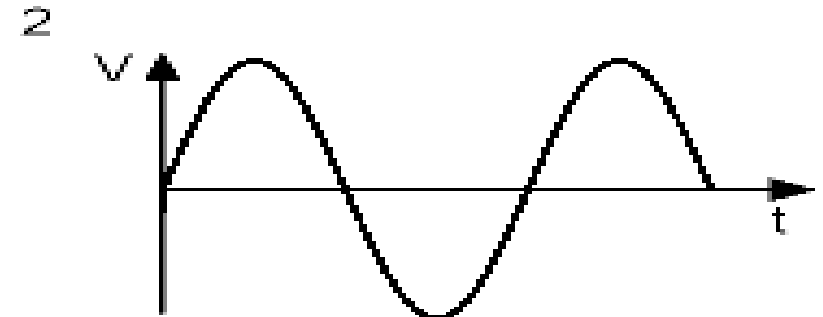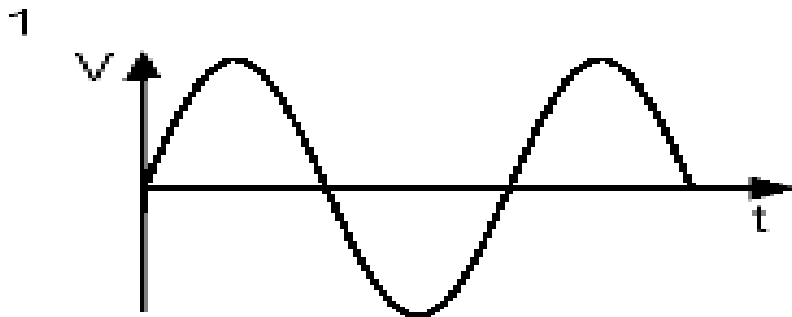Wave forms at various points in a Regulated power supply



Rectification

- Rectification is a process of converting the alternating quantity (voltage or current) into a corresponding direct quantity (voltage or current).
- The **input to a rectifier is AC** whereas its **output is unidirectional or DC.**


Rectifiers

- Rectifier is an electronic device which is used for converting an alternating quantity (Voltage or current) into unidirectional i.e. DC quantity (Voltage or current).
- **Block diagram of Rectifier:**


Need of Rectification

- Every electronic circuit such as amplifiers, needs a DC power source for its operation.
- This DC voltage has to be obtained from AC supply.
- For this the AC supply has to be reduced () Stepped down first using a Step down transformer and then converted to dc by using rectifier.


Types of Rectifier

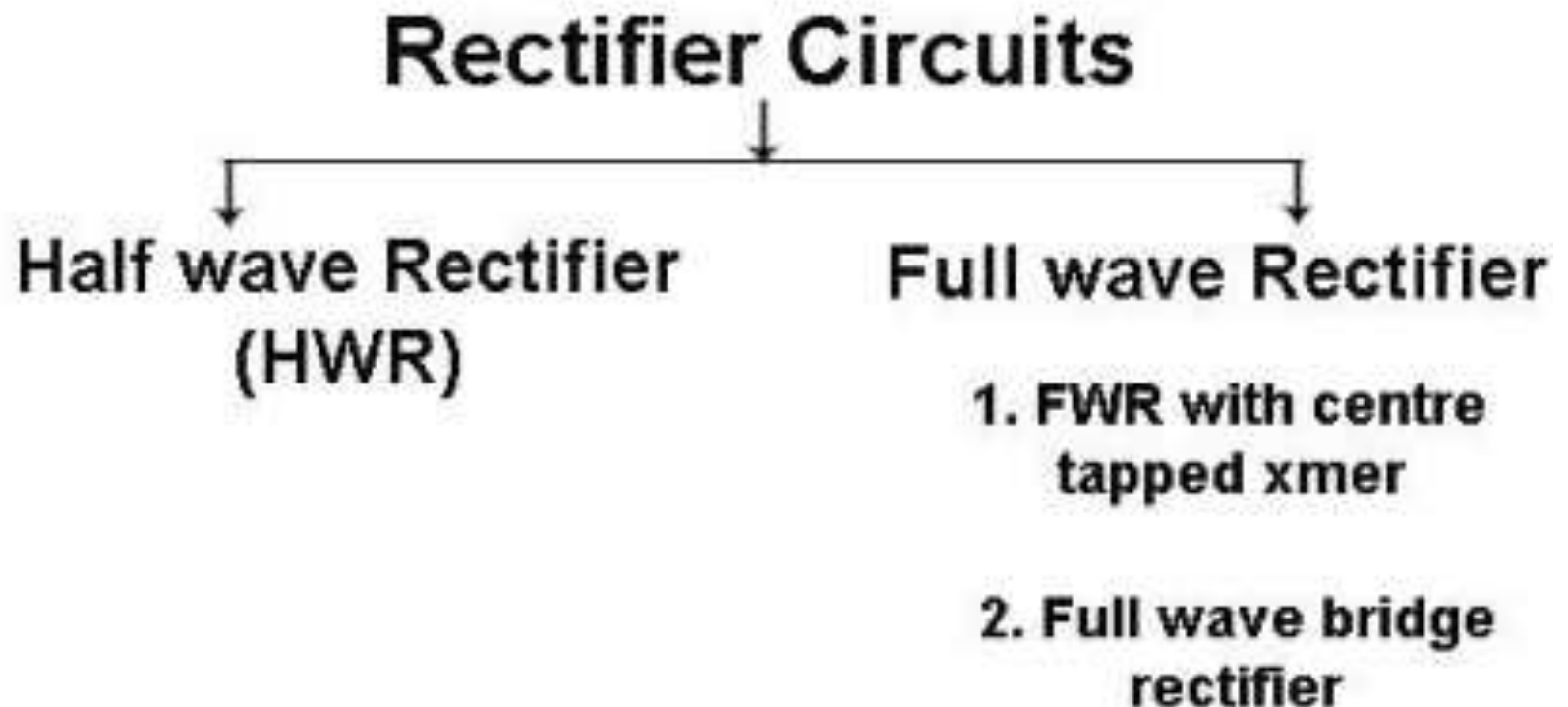

Half Wave Rectifier

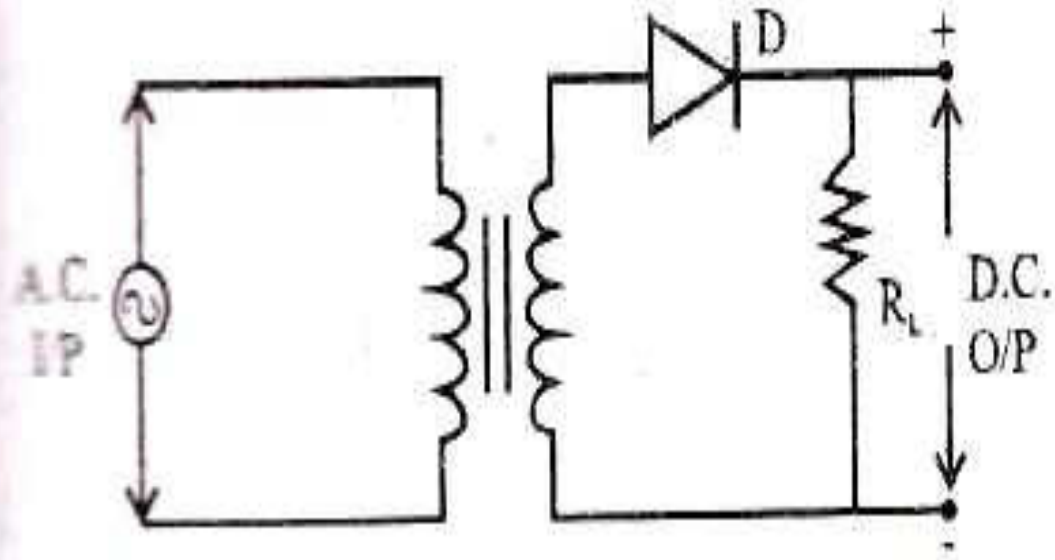


a) Half wave Rectifier


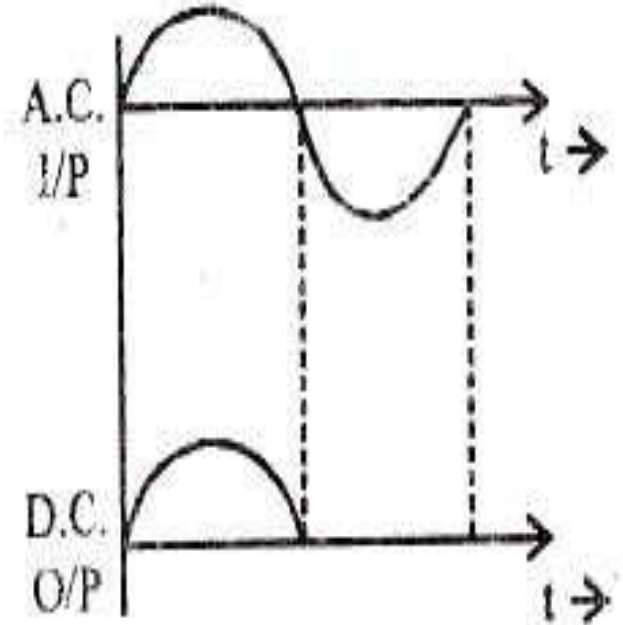


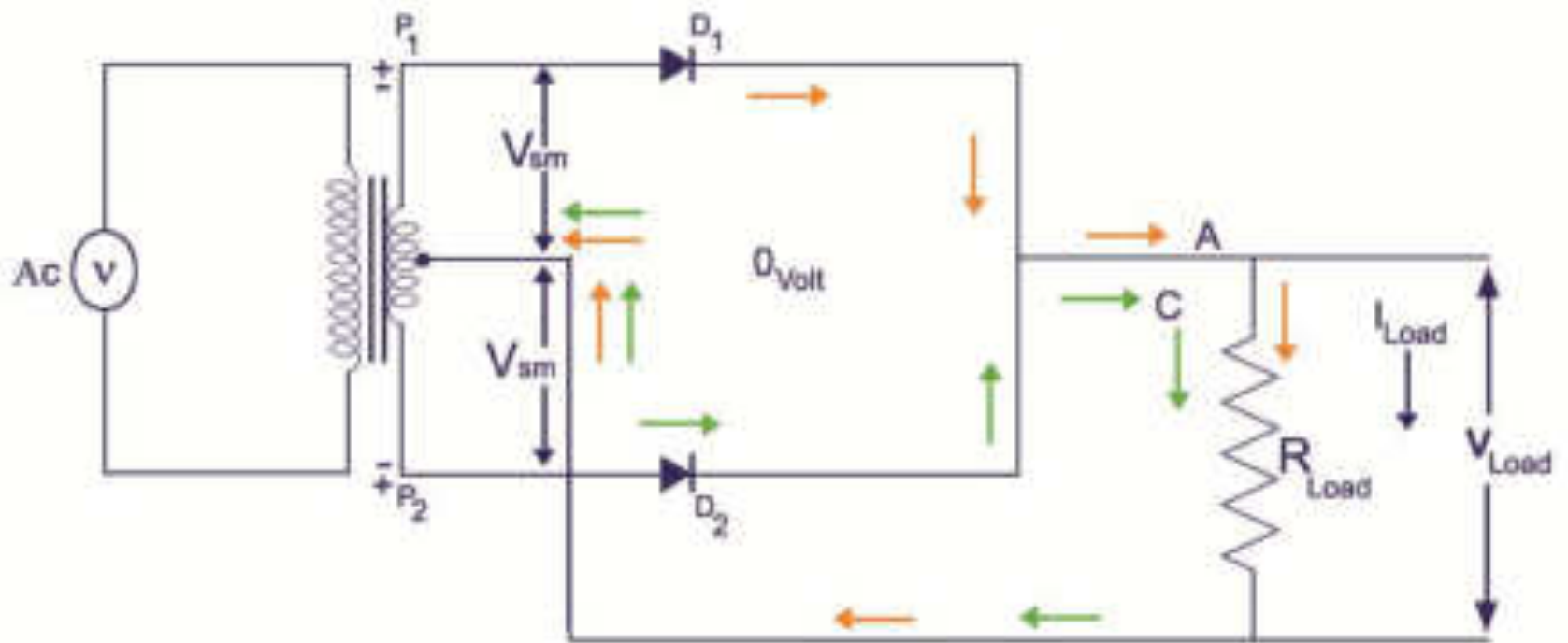b) Wave forms


Full Wave Rectifier (Center Tapped Transformer)



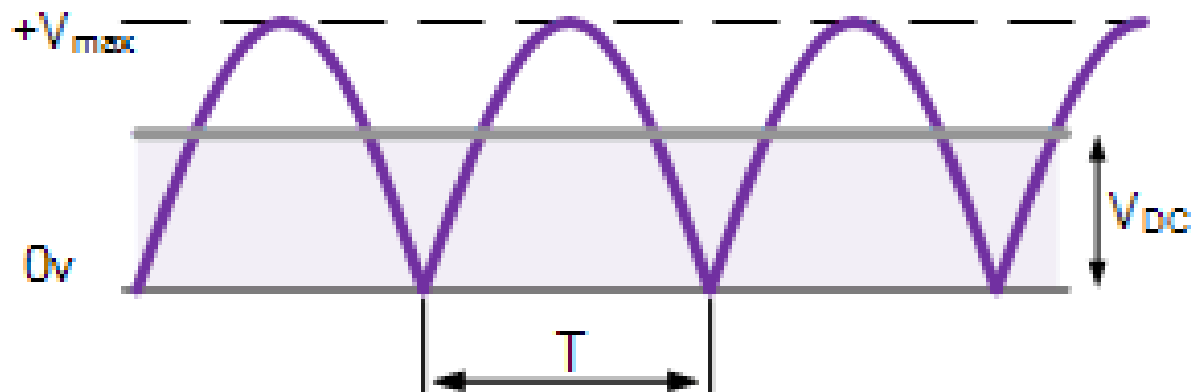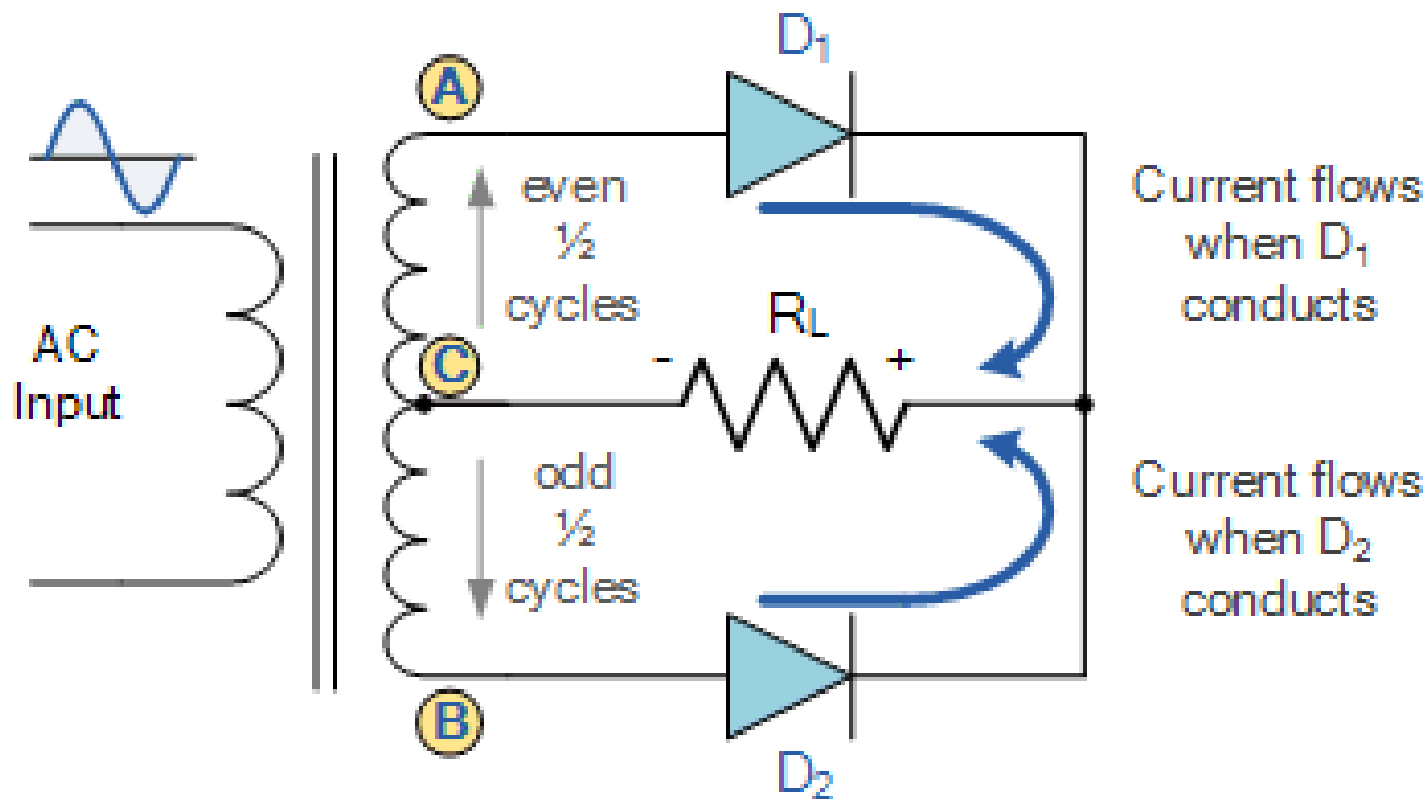
CENTRE - TAP FULL- WAVE RECTIFIER CIRCUIT




Resultant Output Waveform

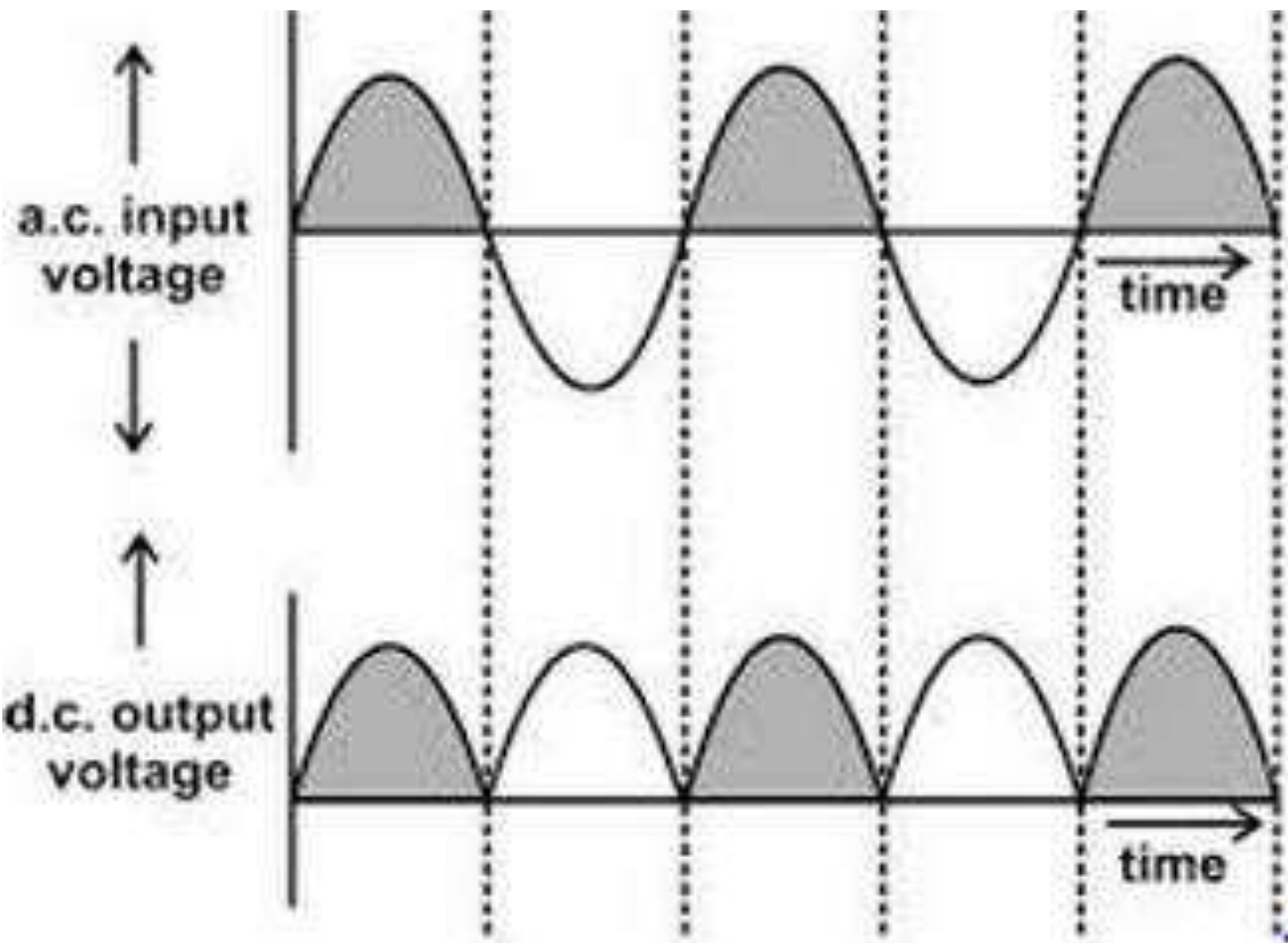

Full Wave Rectifier (Bridge)

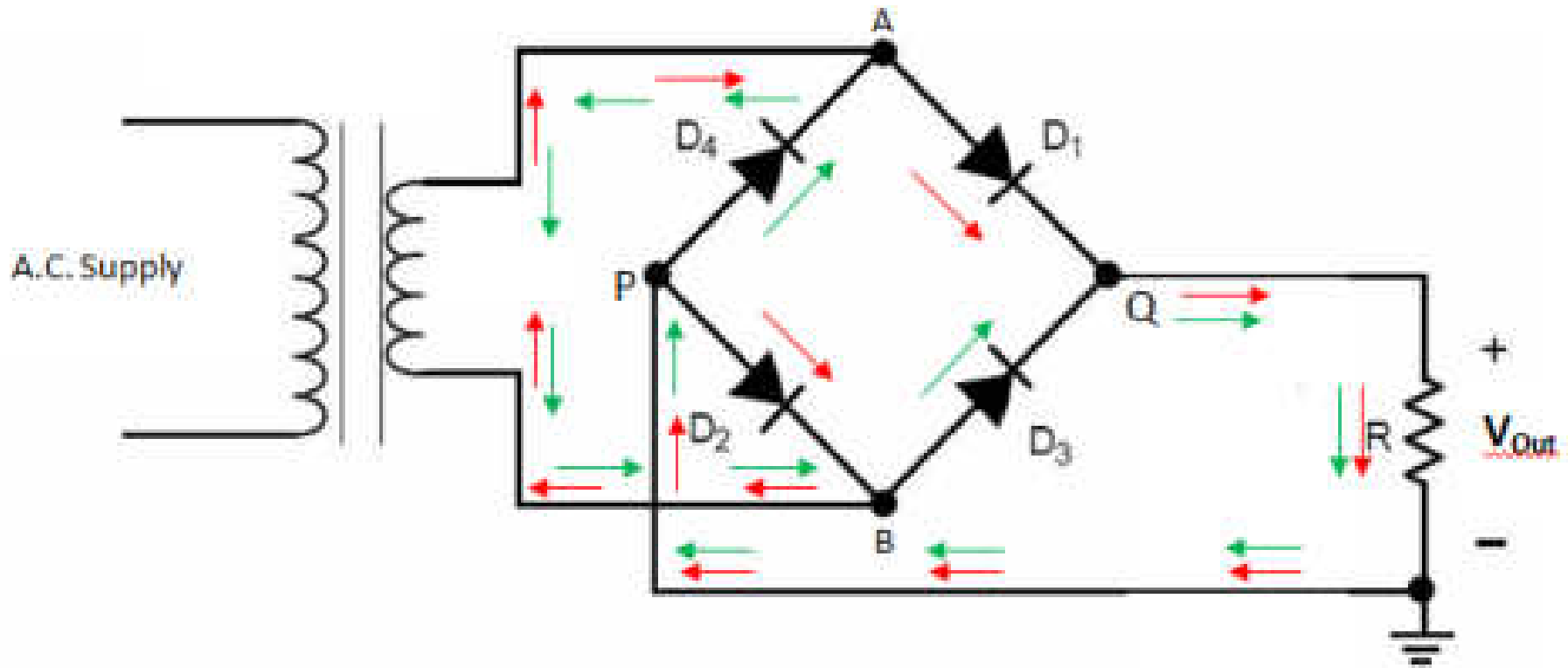


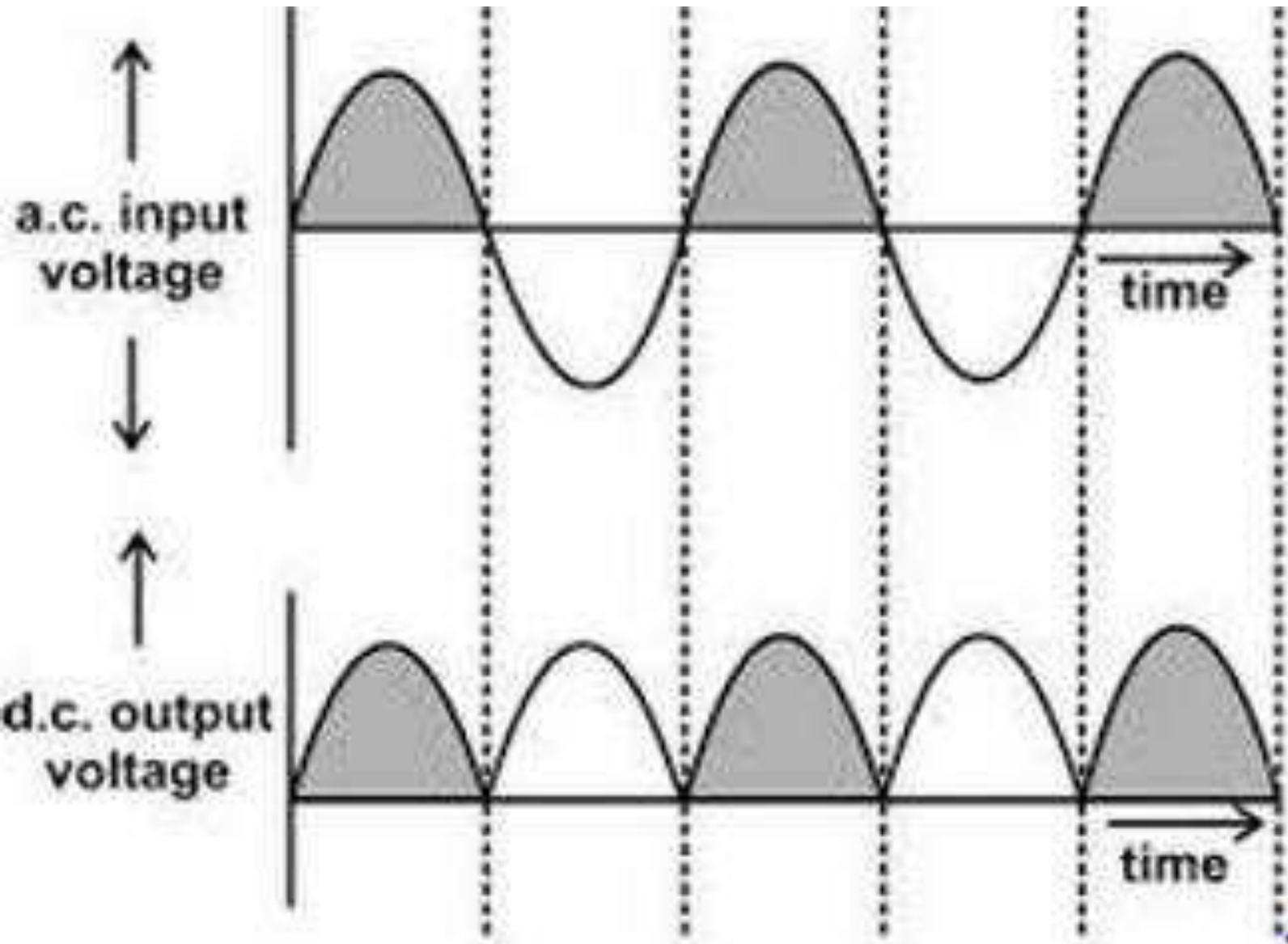

[For more detail contact us](#)

Operational amplifier

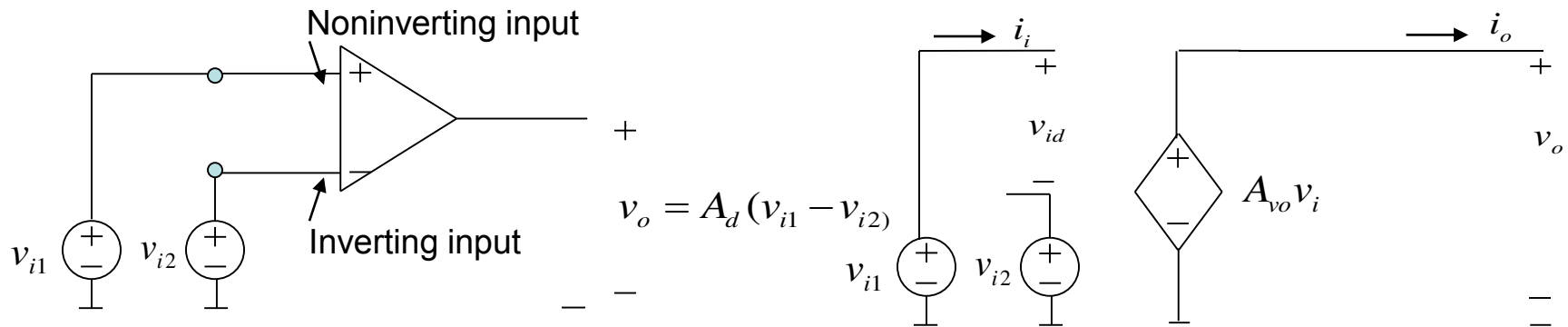- Operational amplifier, or simply *OpAmp* refers to an integrated circuit that is employed in wide variety of applications (including voltage amplifiers)




- OpAmp is a differential amplifier having both inverting and non-inverting terminals
- What makes an ideal OpAmp
 - infinite input impedance
 - Infinite open-loop gain for differential signal
 - zero gain for common-mode signal
 - zero output impedance
 - Infinite bandwidth

Summing point constraint

- In a *negative feedback* configuration, the feedback network returns a fraction of the output to the *inverting input terminal*, forcing the differential input voltage toward zero. Thus, the input current is also zero.
- We refer to the fact that differential input voltage and the input current are forced to zero as the summing point constraint
- Steps to analyze ideal OpAmp-based amplifier circuits
 - Verify that negative feedback is present
 - Assume summing point constraints
 - Apply Kirchhoff's law or Ohm's law

Some useful amplifier circuits

- Inverting amplifier

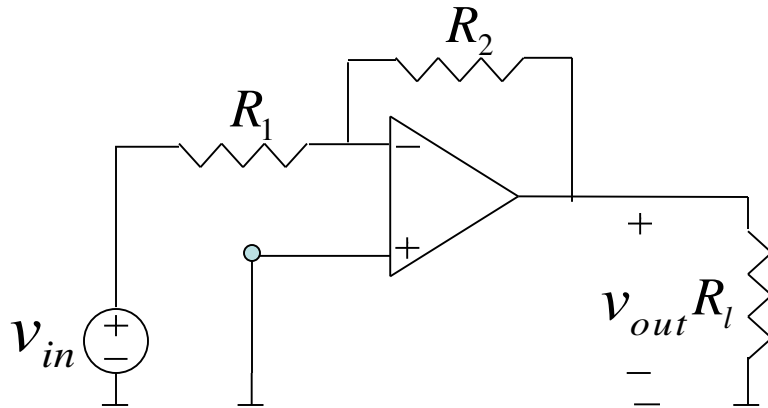


$$A_v = v_{out} / v_{in} = -R_2 / R_1$$

$$Z_{in} = R_1$$

$$Z_{out} = 0$$

- Noninverting amplifier

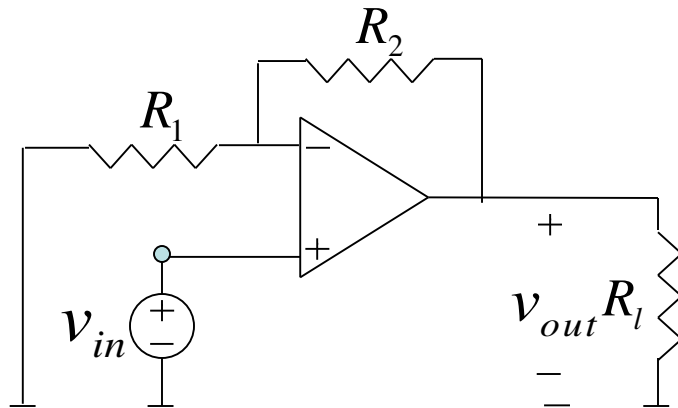

$$A_v = v_{out} / v_{in} = 1 + R_2 / R_1$$

$$Z_{in} = \infty$$

$$Z_{out} = 0$$

- Voltage follower if $R_2 = 0$ and R_1 open circuit (unity gain)

Amplifier design using OpAmp

- Resistance value of resistor used in amplifiers are preferred in the range of (1K,1M)ohm (this may change depending on the IC technology). Small resistance might induce too large current and large resistance consumes too much chip area.

OpAmp non-idealities I

- *Nonideal properties in the linear range of operation*

- Finite input and output impedance

- Finite gain and bandwidth limitation

- ✓ Generally, the open-loop gain of OpAmp as a function of frequency is

$$A_{ol}(f) = \frac{A_{0ol}}{1 + j(f / f_{bol})}, \text{ } A_{0ol} \text{ is open-loop gain at DC,}$$

f_{bol} is open-loop break frequency, also called dominant pole

- ✓ Closed-loop gain versus frequency for non-inverting amplifier

$$A_{cl(f)} = \frac{A_{0cl}}{1 + j(f / f_{bcl})}, \text{ } A_{0cl} = \frac{A_{0ol}}{1 + \beta A_{0ol}}, \text{ } f_{bcl} = f_{bol}(1 + \beta A_{0ol}), \text{ } \beta = \frac{R_1}{R_1 + R_2}$$

- ✓ Gain-bandwidth product:

$$f_t = A_{0cl} f_{bcl} = A_{0ol} f_{bol}, \text{ where } f_t \text{ is called unity-gain frequency}$$

- ✓ Closed-loop bandwidth for both non-inverting and inverting amplifier



$$f_{bcl} = \frac{f_t}{1 + R_2 / R_1} = \frac{A_{0ol} f_{bol}}{1 + R_2 / R_1}$$

OpAmp non-idealities II

- Output voltage swing: real OpAmp has a maximum and minimum limit on the output voltages
 - OpAmp transfer characteristic is nonlinear, which causes clipping at output voltage if input signal goes out of linear range
 - The range of output voltages before clipping occurs depends on the type of OpAmp, the load resistance and power supply voltage.
- Output current limit: real OpAmp has a maximum limit on the output current to the load
 - The output would become clipped if a small-valued load resistance drew a current outside the limit
- Slew Rate (SR) limit: real OpAmp has a maximum rate of change of the output voltage magnitude
 - limit $\left| \frac{dv_o}{dt} \right| \leq SR$
 - SR can cause the output of real OpAmp very different from an ideal one if input signal frequency is too high
 - Full Power bandwidth: the range of frequencies for which the OpAmp can produce an undistorted sinusoidal output with peak amplitude equal to the maximum allowed voltage output

$$f_{FP} = \frac{SR}{2\pi v_{o\max}}$$


Slew Rate

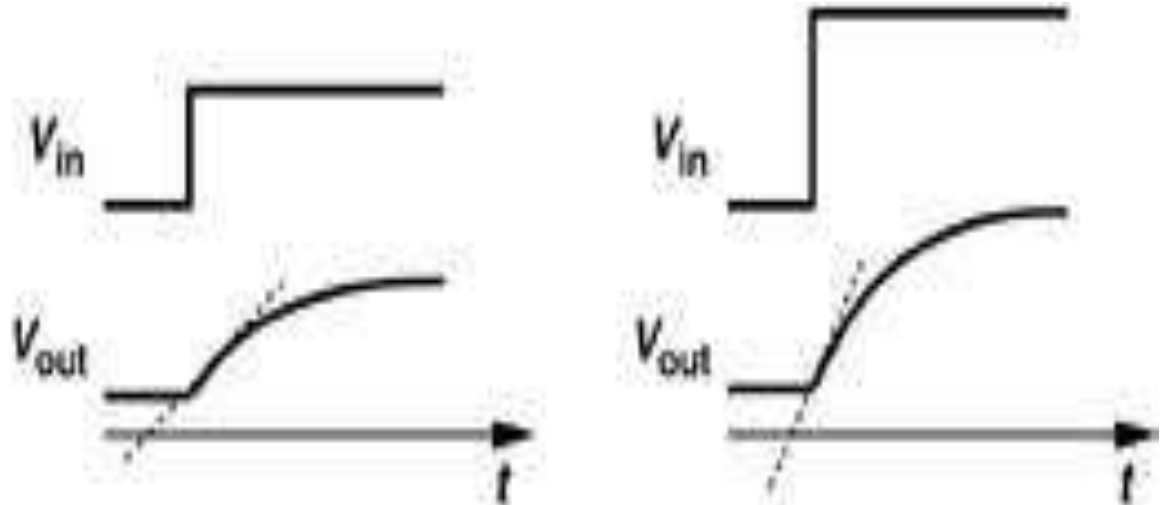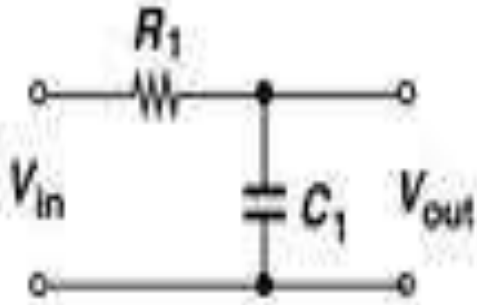

- ❑ Linear RC Step Response: the slope of the step response is proportional to the final value of the output, that is, if we apply a larger input step, the output rises more rapidly.
- ❑ If V_{in} doubles, the output signal doubles at every point, therefore a twofold increase in the slope.
- ❑ But the problem in real OpAmp is that this slope can not exceed a certain limit.


OpAmp non-idealities III

- DC imperfections: *bias current, offset current and offset voltage*
 - bias current I_B : the average of the dc currents flow into the noninverting terminal I_{B+} and inverting terminal I_{B-} , $I_B = 1/2(I_{B+} + I_{B-})$
 - offset current: the half of difference of the two currents, $I_{off} = 1/2(I_{B+} - I_{B-})$
 - offset voltage: the DC voltage needed to model the fact that the output is not zero with input zero, V_{off}
- The three DC imperfections can be modeled using DC current and voltage sources

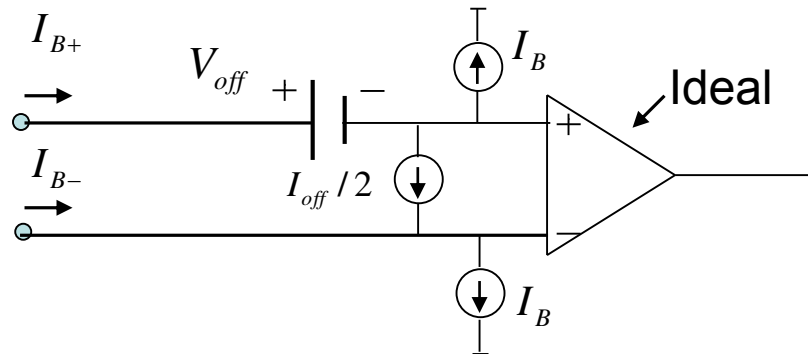

- The effects of DC imperfections on both inverting and noninverting amplifier is to add a DC voltage to the output. It can be analyzed by considering the extra DC sources assuming an otherwise ideal OpAmp
- It is possible to cancel the bias current effects. For the inverting amplifier, we can add a resistor $R = R_1 // R_2$ to the non-inverting terminal


DC offset of an differential pair

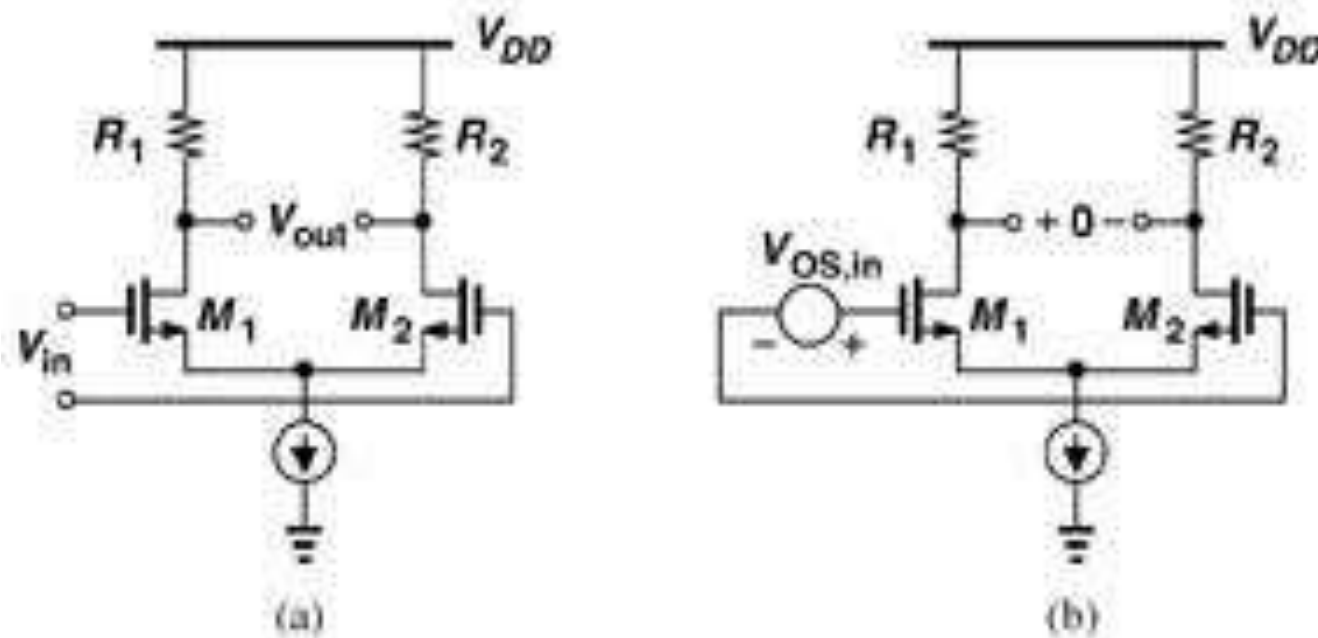

- ❑ When $V_{in}=0$, V_{out} is NOT 0 due to mismatch of transistors in real circuit design.
- ❑ It is more meaningful to specify input-referred offset voltage, defined as $V_{os,in}=V_{os,out} / A$.
- ❑ Offset voltage may causes a DC shift of later stages, also causes limited precision in signal comparison.

Behavioral modeling of OpAmp

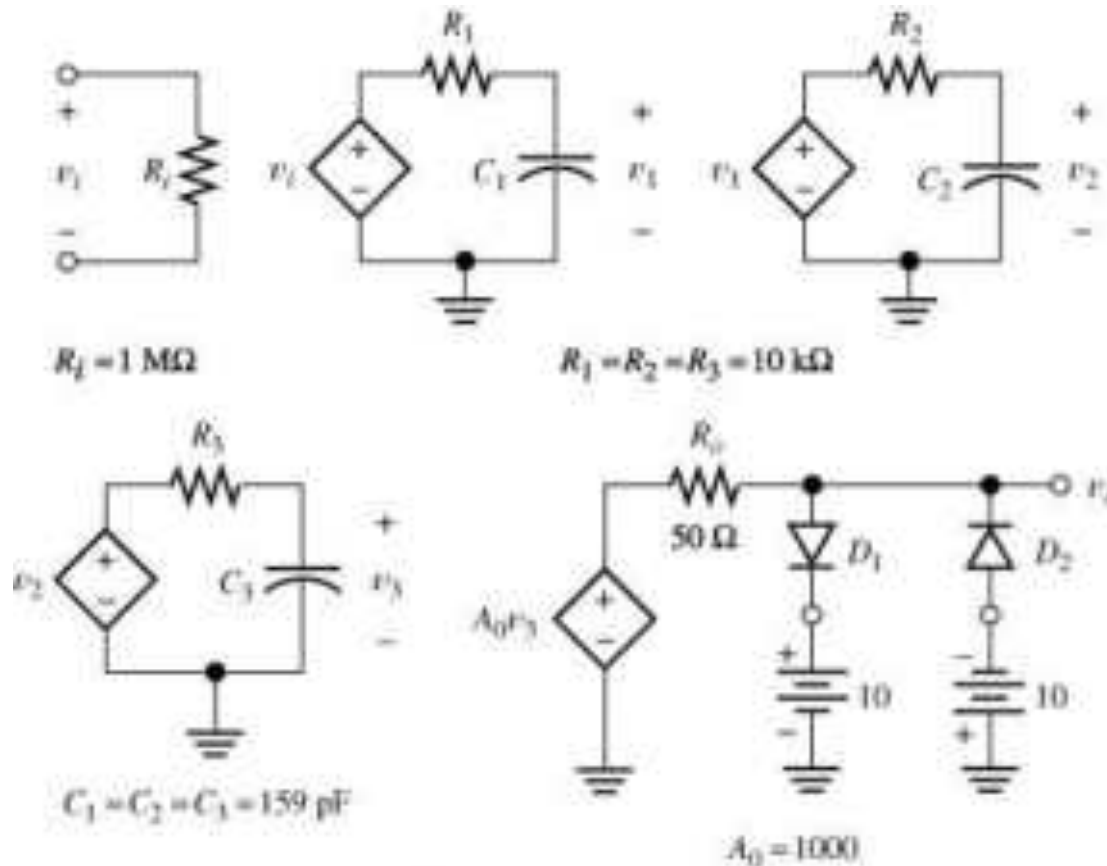
- ❑ Behavioral models is preferred to include as many non-idealities of OpAmp as possible.
- ❑ They are used to replace actual physical OpAmp for analysis and fast simulation.



(a) Circuit model of amplifier

Important amplifier circuits I

- Inverting amplifier

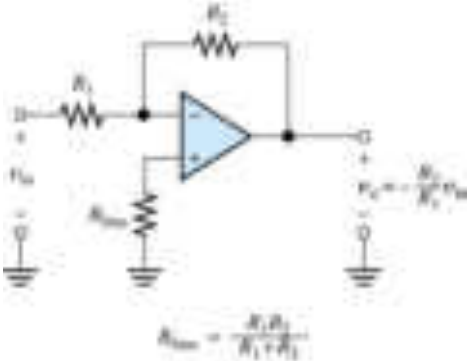


$$A_v = -R_2 / R_1$$

$$Z_{in} = R_1$$

$$Z_{out} = 0$$

- Noninverting amplifier

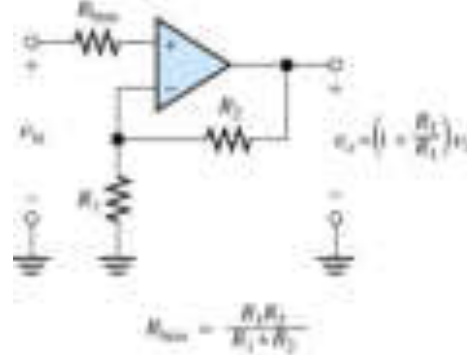


$$A_v = 1 + R_2 / R_1$$

$$Z_{in} = \infty$$

$$Z_{out} = 0$$

- AC-coupled inverting amplifier

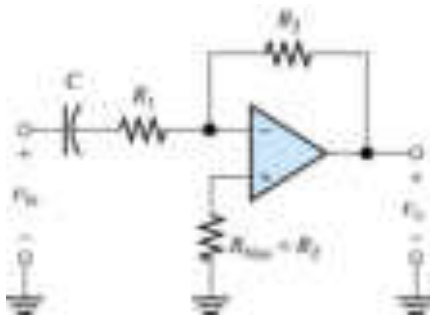


$$A_v = -R_2 / R_1$$

$$Z_{in} = R_1$$

$$Z_{out} = 0$$

- AC-coupled noninverting amplifier

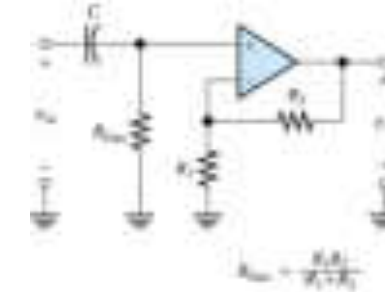


$$A_v = 1 + R_2 / R_1$$

$$Z_{in} = R_{bias}$$

$$Z_{out} = 0$$

- Summing amplifier

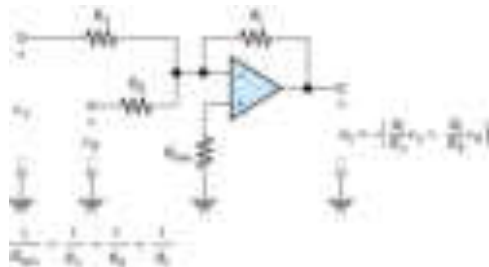


$$A_v = -R_f / R_{A/B}$$

$$Z_{in1} = R_A \text{ for } v_A$$

$$Z_{in2} = R_B \text{ for } v_B$$

$$Z_{out} = 0$$

- Bootstrap AC-coupled voltage follower

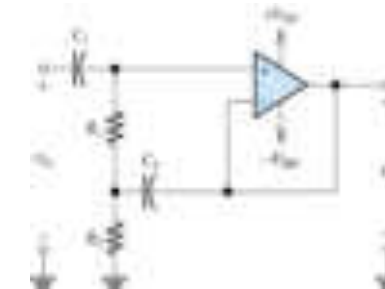


$$A_v = 1$$

$$Z_{in} = \infty$$

$$Z_{out} = 0$$

Important amplifier circuits II


- Differential amplifier

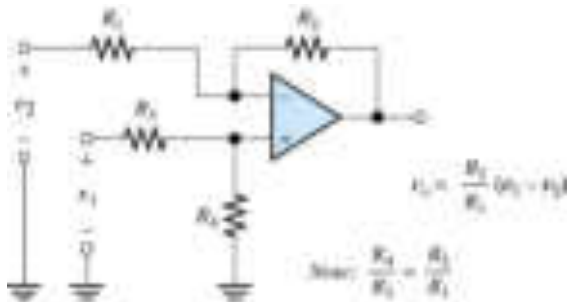

$$Z_{in} = R_3 + R_4 \text{ for } v_1$$

$$Z_{out} = 0$$

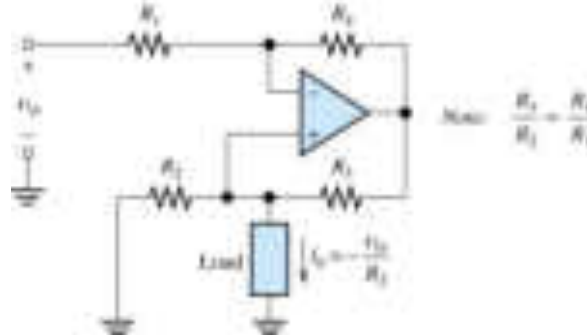- Howland voltage-to-current converter for grounded load




$$G_m = -1/R_2$$

$$Z_{in} = R_1 R_2 / (R_2 + R_L)$$

$$Z_{out} = \infty$$


- Instrumentation quality Diff Amp

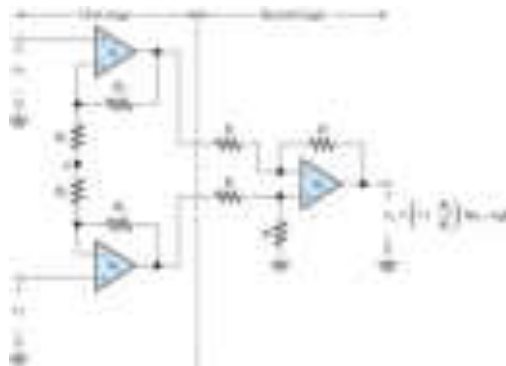

$$Z_{in} = \infty$$

$$Z_{out} = 0$$

- Current-to-voltage amplifier

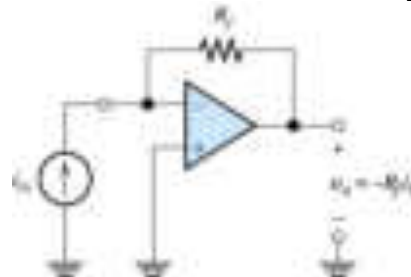


$$R_m = -R_f$$

$$Z_{in} = 0$$

$$Z_{out} = 0$$

- Voltage-to-current converter

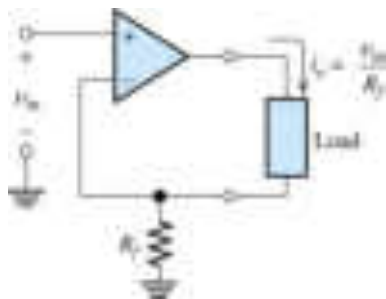


$$G_m = i_o / v_{in} = -1/R_f$$

$$Z_{in} = \infty$$

$$Z_{out} = \infty$$

- Current amplifier

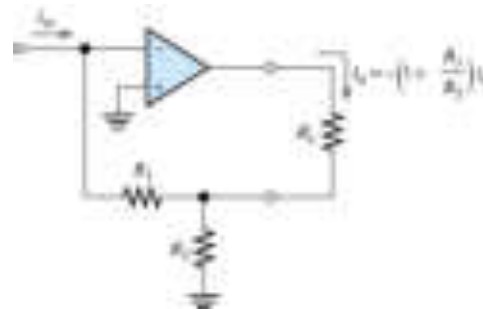


$$A_{vi} = -(1 + R_2 / R_1)$$

$$Z_{in} = 0$$


$$Z_{out} = \infty$$

Important amplifier circuits III

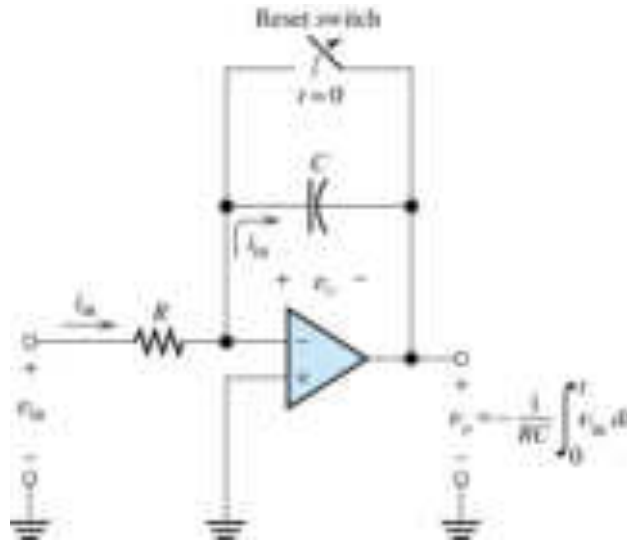- Integrator circuit: produces an output voltage proportional to the running time integral of the input signal



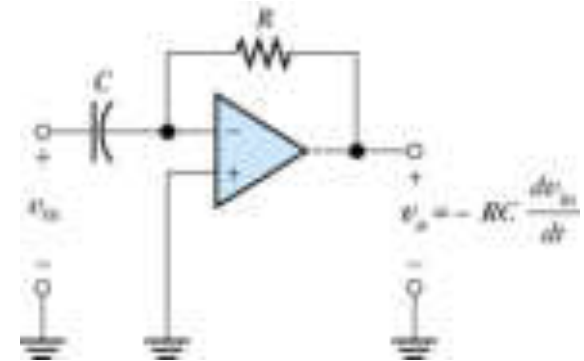- Differentiator circuit: produces an output proportional to the time derivative of the input voltage




Bipolar Junction transistor




Holes and electrons
determine device characteristics

Three terminal device

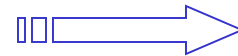


Control of two terminal currents


How can we make a BJT from a pn diode?

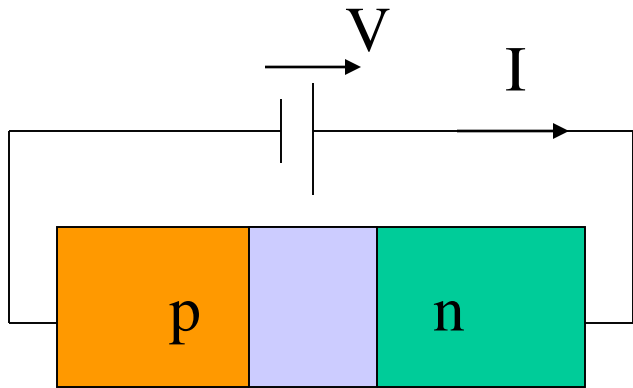

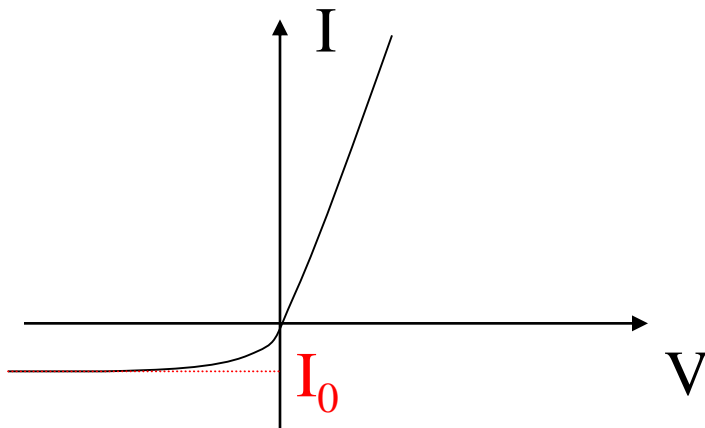- Take pn diode
- Remember reverse bias characteristics
- Reverse saturation current: I_0



How can we make a BJT from a pn diode?

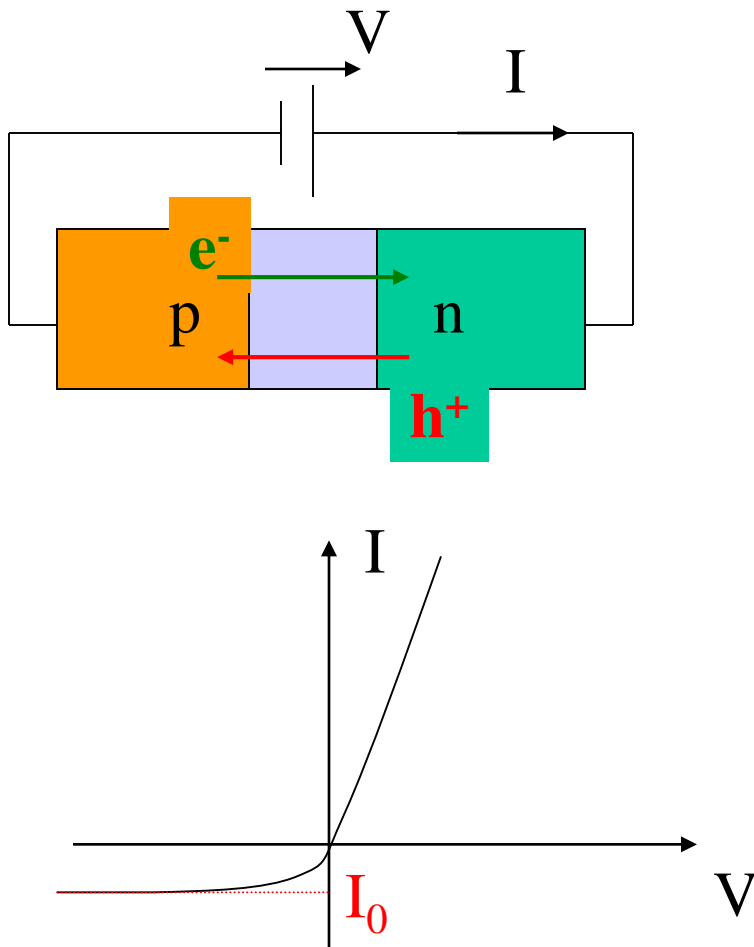


- Take pn diode
- Remember reverse bias characteristics
- Reverse saturation current: I_0
Caused by minority carriers swept across the junction
- n_p and p_n low
→ I_0 small

Thus:

A forward biased p^+n diode is a good hole injector

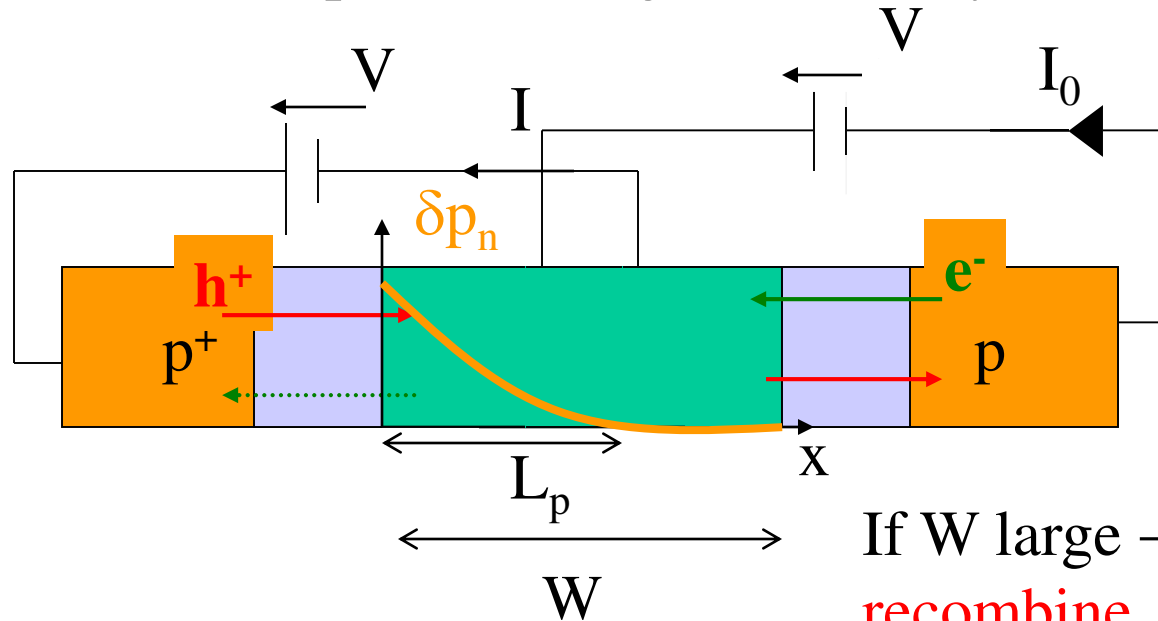
A reverse biased np diode is a good minority carrier collector



If W large \rightarrow holes
recombine

Excess hole
concentration reduces
exponentially in W to
some small value.


Carrier flow in BJTs

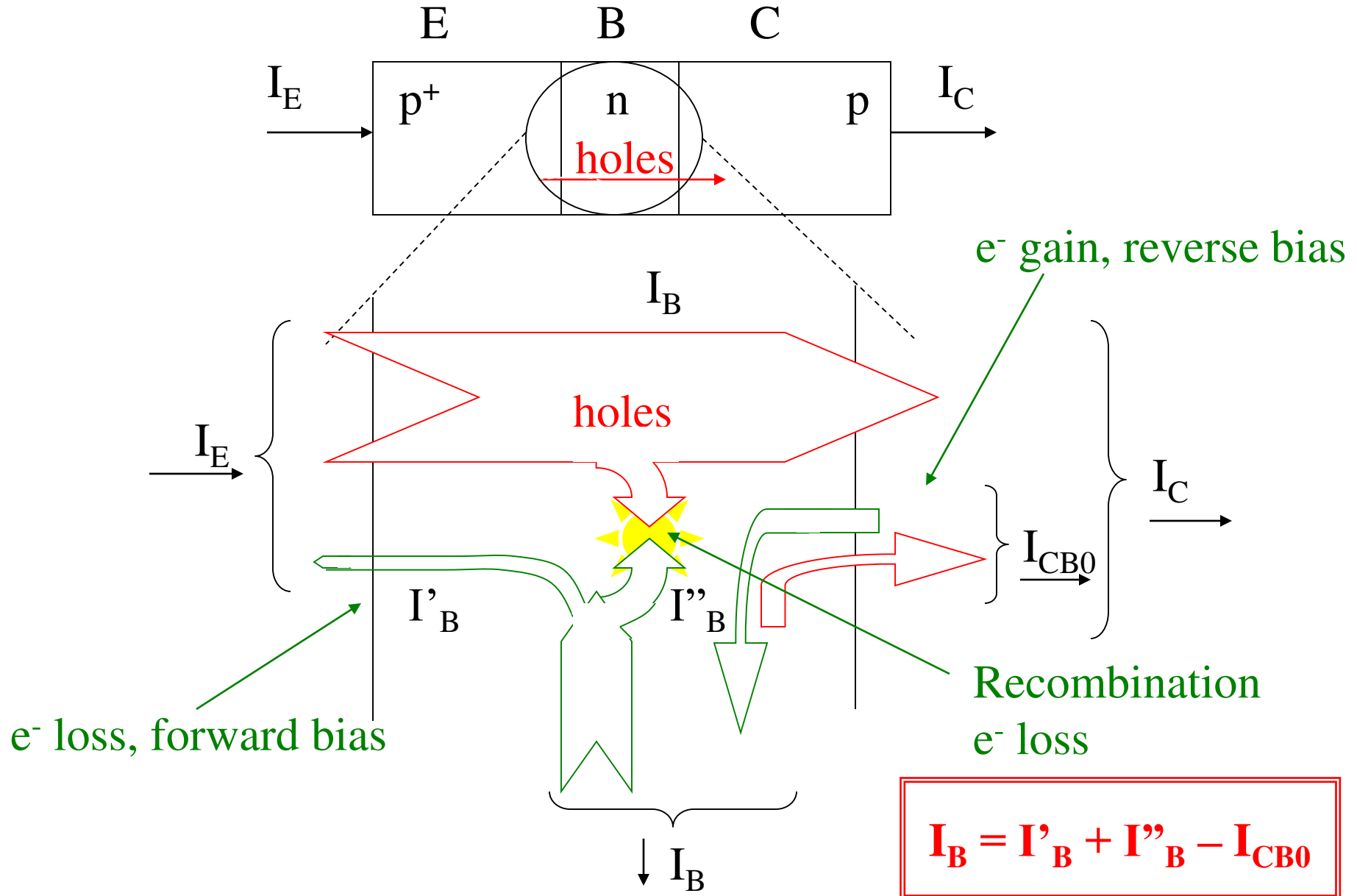

Control by base current : ideal case.

Based upon space charge neutrality


Electrostatically neutral

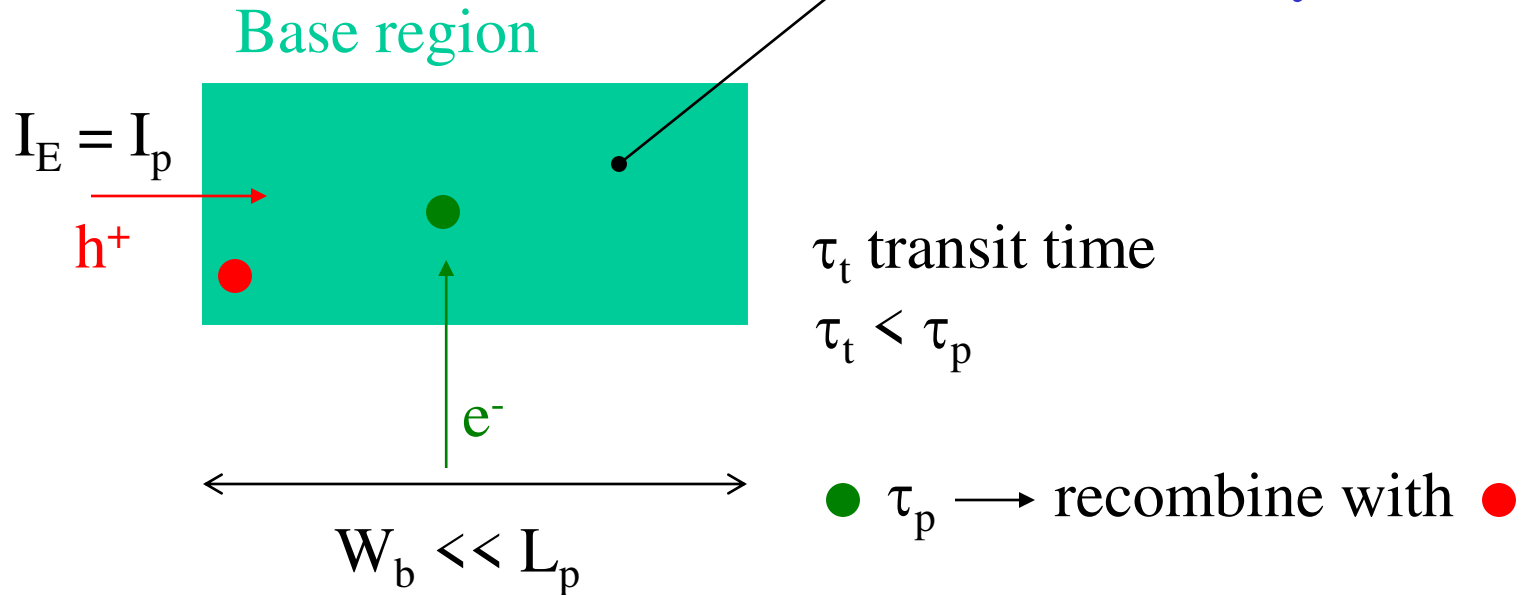

Based on the given timescales, holes can pass through the narrow base before a supplied electron recombines with one hole: $i_c/i_b = \tau_p/\tau_t$

The electron supply from the base contact controls the forward bias to ensure charge neutrality!

How good is the transistor?

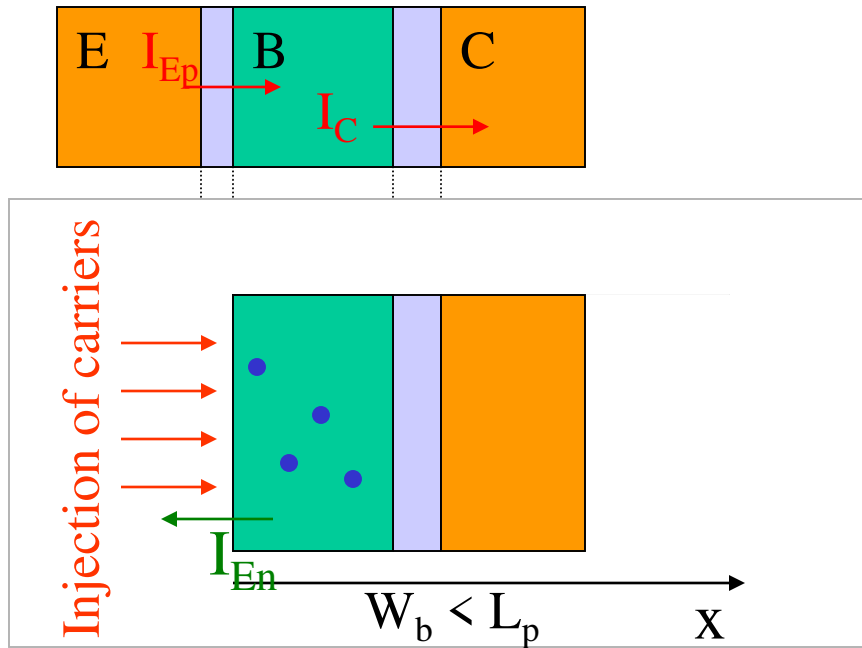

- Wish list:
- $I_{Ep} \gg I_{En}$
or $\gamma = I_{Ep} / (I_{En} + I_{Ep}) \approx 1$
 γ : emitter injection efficiency
- $I_C \approx I_{Ep}$
or $B = I_C / I_{Ep} \approx 1$
 B : base transport factor
or $\alpha = I_C / I_E \approx 1$
 α : current transfer ratio
- $I_B \approx I_{En} + (1-B) I_{Ep}$
thus $\beta = I_C / I_B = \alpha / (1-\alpha)$
 β : current amplification factor



No amplification!

Amplification!

I_{CB0} ignored

Review 1 – BJT basics

Forward active mode (ON)

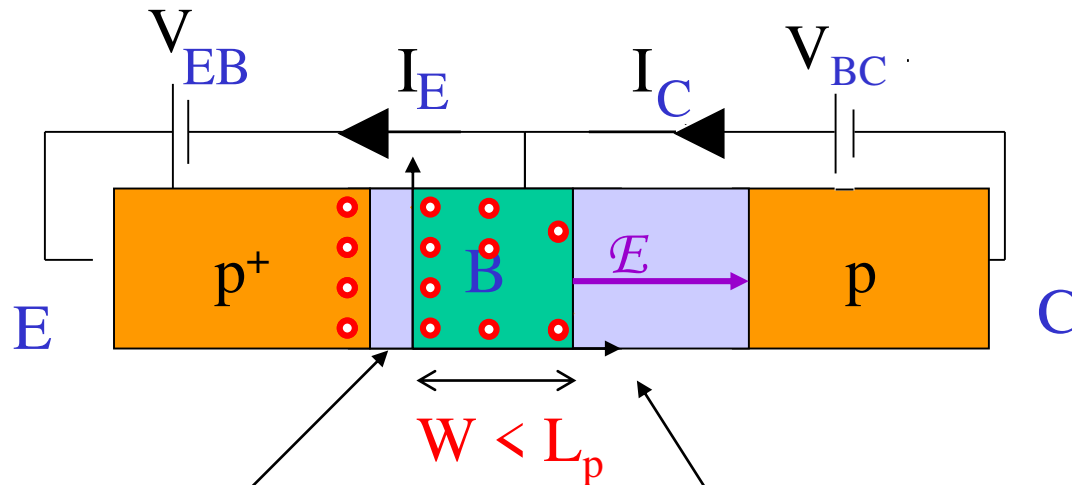
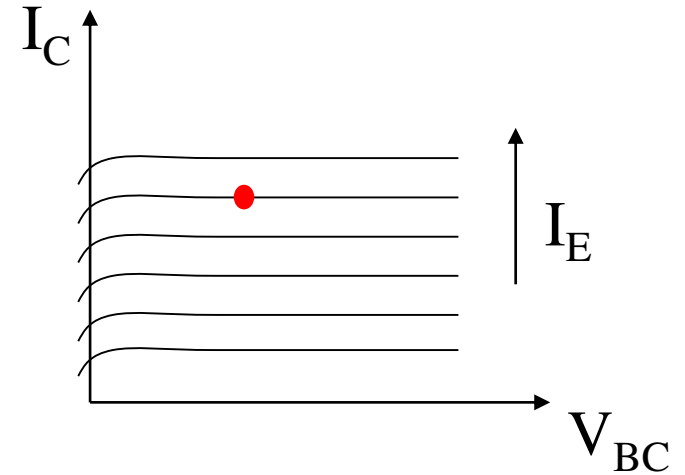


Forward biased p⁺n junction is a **hole injector**

Reverse biased np junction is a **hole collector**

Review 1 – BJT basics

Forward active mode (ON)

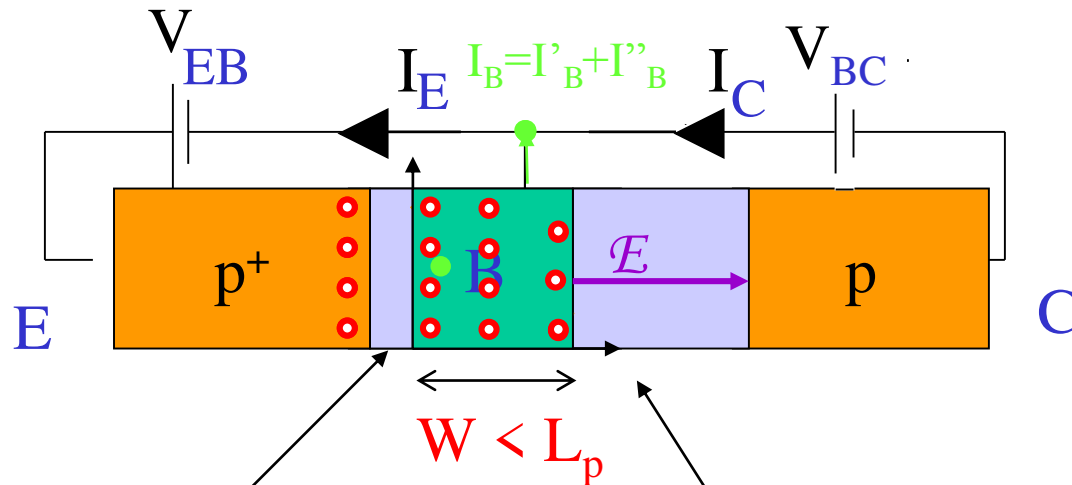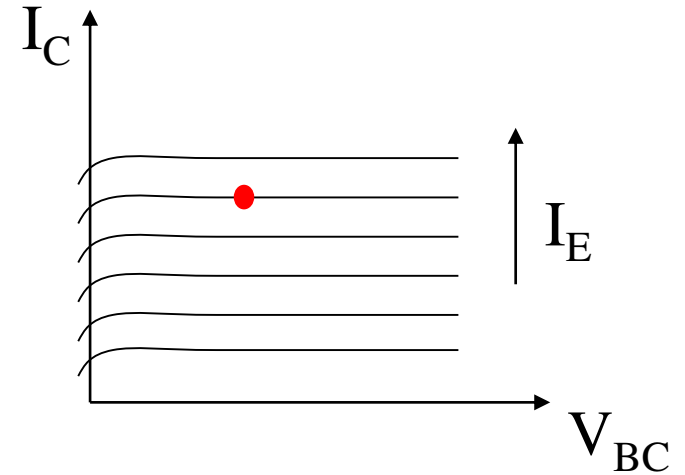

Forward biased p^+n junction is a **hole injector**

Reverse biased np junction is a **hole collector**

Review 2

Amplification?

$$I_B = I'_B + I''_B - I_{CB0}$$

Recombination only case: I'_B , I_{CB0} negligible

$$i_c/i_b = \tau_p/\tau_t$$

$$\beta = \tau_p/\tau_t$$

Carriers supplied by the base current stay much longer in the base: τ_p than the carriers supplied by the emitter and travelling through the base: τ_t .

But in more realistic case: I'_B is not negligible

$$\beta = I_C/I_B$$

With I_B electrons supplied by base = $I'_B = I_n$
 I_C holes collected by the collector = I_p

Currents?

- In order to calculate currents in pn junctions, knowledge of the **variation of the minority carrier** concentration is required in each layer.
- The current flowing through the base will be determined by the excess carrier distribution in the base region.
- **Simple** to calculate when the **short diode approximation** is used: this means *linear variations* of the minority carrier distributions in all regions of the transistor. (**recombination neglected**)
- Complex when **recombination** in the base is also taken into account: then *exponential* based minority carrier concentration in base.

Narrow base: **no** recombination: I_p

→ minority carrier density gradient in the base

$$\Delta p_E = p_{n0}(e^{eV_{EB}/kT} - 1) \approx p_{n0} e^{eV_{EB}/kT}$$

$$\Delta p_C = p_{n0}(e^{-e|V_{BC}|/kT} - 1) \approx -p_{n0}$$


Linear variation of excess carrier concentration:

$$\delta p(x) = Ax + B$$

$$A = \frac{\Delta p_E - \Delta p_C}{-W_b} \approx -\frac{\Delta p_E}{W_b}$$

$$B = \Delta p_E + \Delta p_C \approx \Delta p_E$$
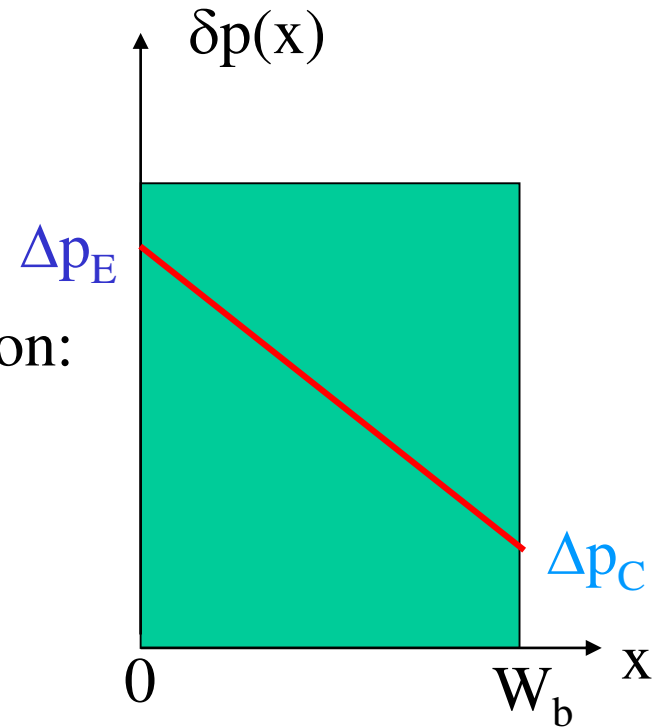
$$\delta p(x) = \Delta p_E \left(1 - \frac{x}{W_b} \right)$$



Note: no recombination

Collector current: I_p

Diffusion current: $I_p = -eAD_p \frac{d\delta p(x)}{dx}$

$$\frac{d\delta p(x)}{dx} = -\frac{\Delta p_E}{W_b}$$

Hole current: $I_p = eAD_p \frac{\Delta p_E}{W_b} = \frac{eAD_p p_{n0} e^{\left(\frac{eV_{EB}}{kT}\right)}}{W_b}$

Collector current $I_C = I_p$ No recombination, thus all injected holes across the BE junction are collected.

Base current??

Emitter current


The emitter current is the total current flowing through the base emitter contact since $I_E = I_C + I_B$ (current continuity)

Emitter current:
$$I_E = I_n + I_p = eA \left(\frac{D_n n_{p0}}{x_e} + \frac{D_p p_{n0}}{W_B} \right) e^{\left(\frac{eV_{EB}}{kT} \right)}$$

Current gain:
$$\beta = \frac{I_C}{I_B} = \frac{I_p}{I_n} = \frac{D_p p_{n0} x_e}{D_n n_{p0} W_b}$$

Non-ideal effects in BJTs


- Base width modulation

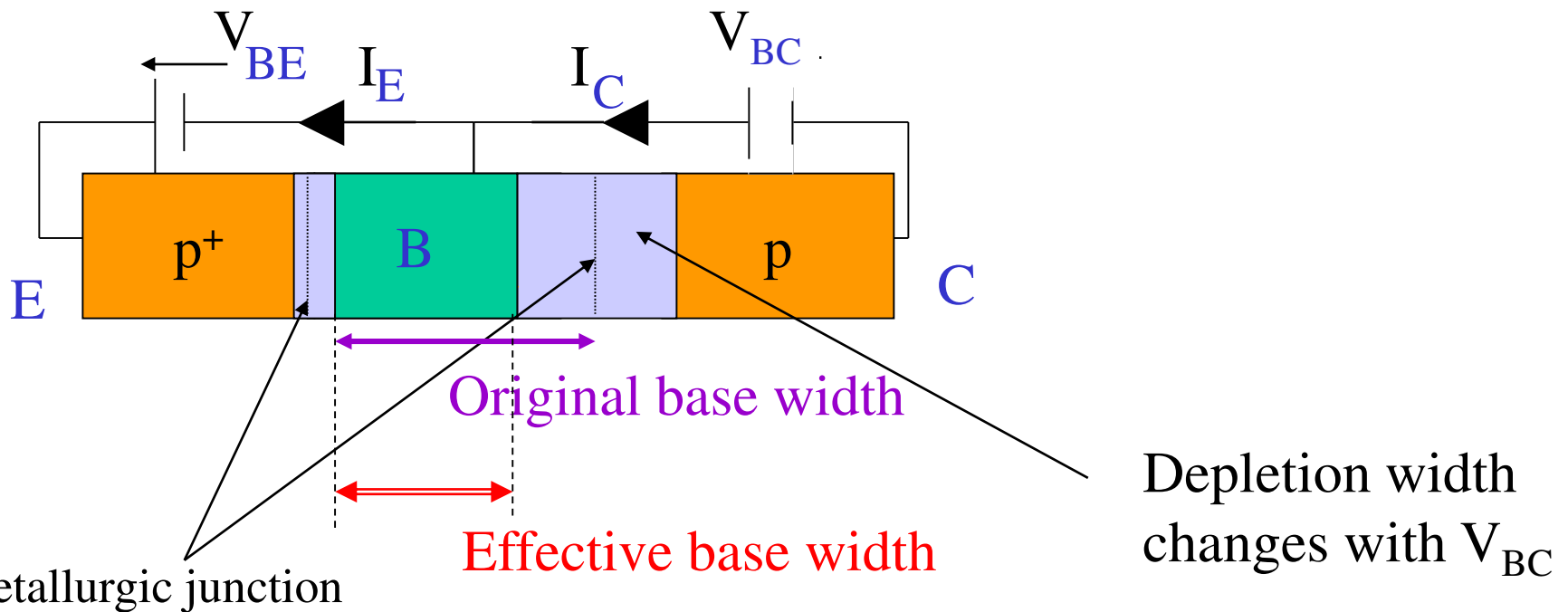






Conclusions


- Characteristics of bipolar transistors are based on **diffusion** of **minority** carriers in the **base**.
- Diffusion is based on **excess carrier** concentrations:
 - $\delta p(x)$
- The base of the BJT is very small:
 - $\delta p(x) = C_1 e^{x/L_p} + C_2 e^{-x/L_p}$
- Base width modulation changes output impedance of BJT.

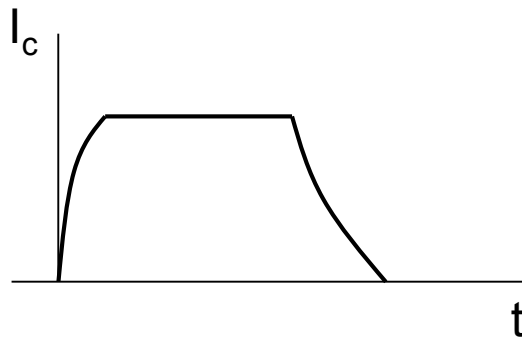
Transistor switching




 p-type material
 n-type material

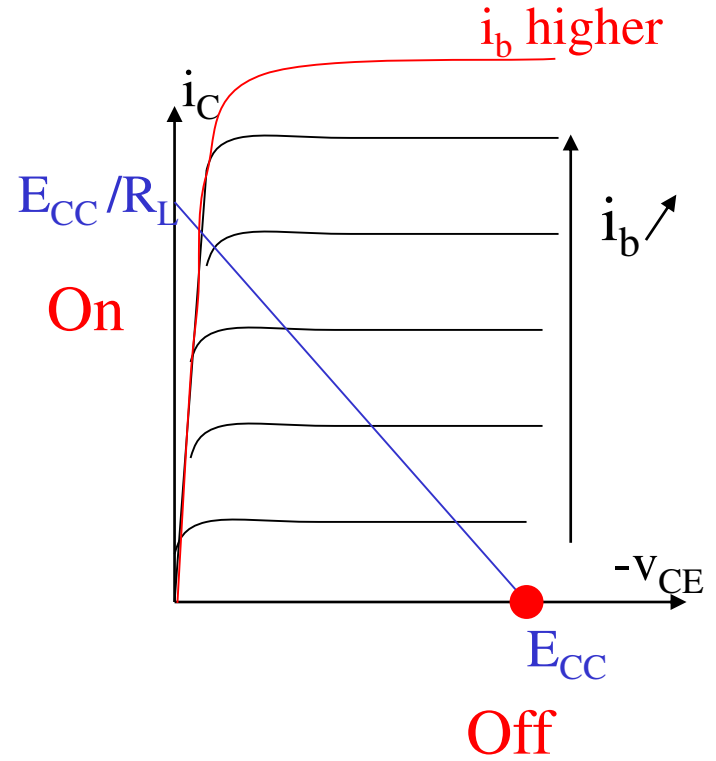
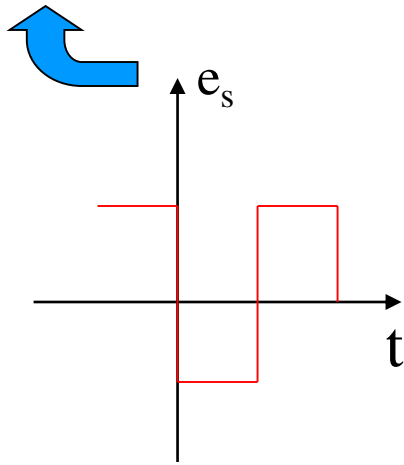
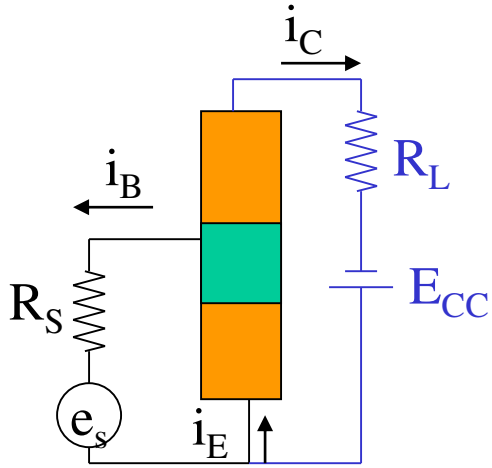


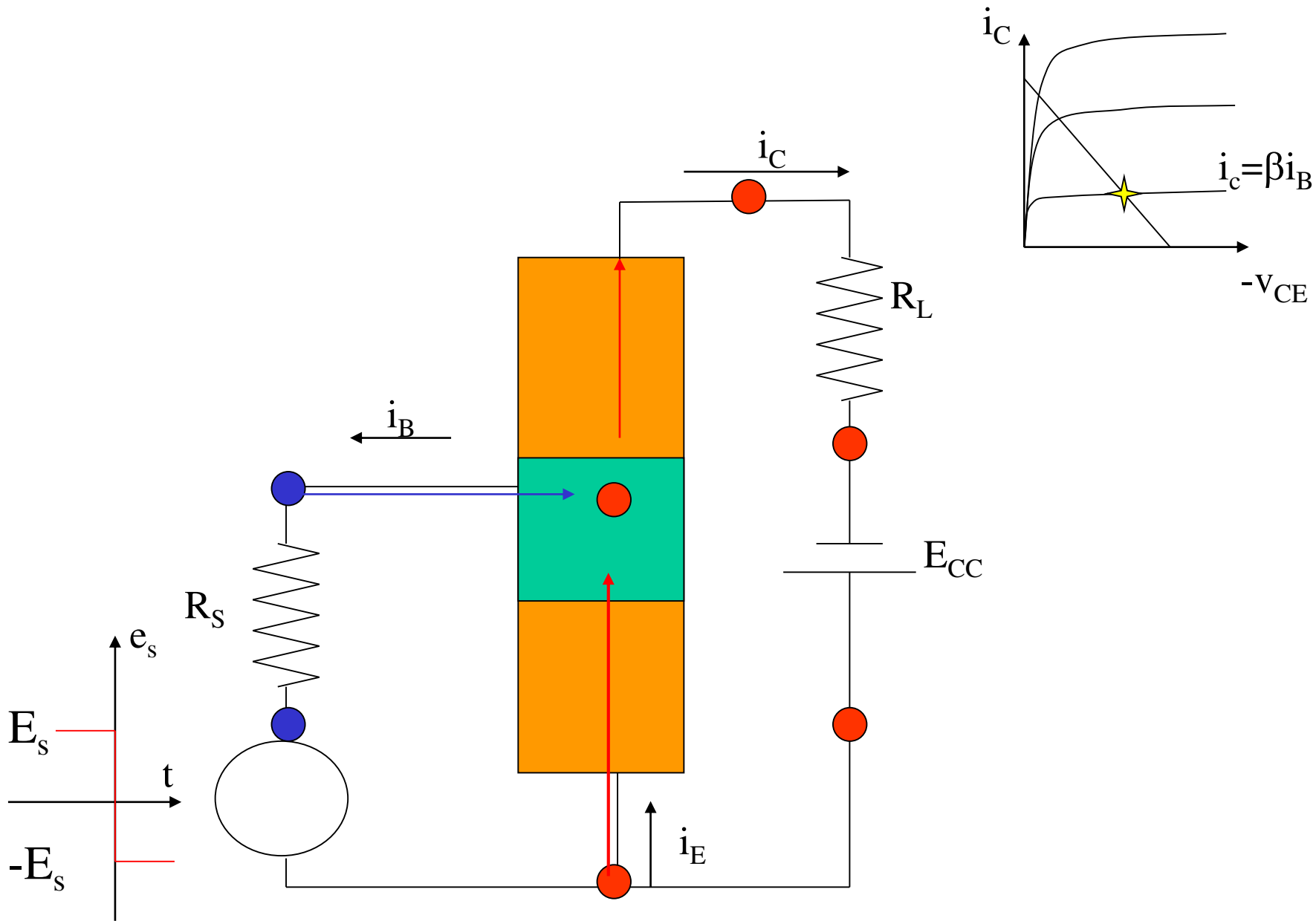

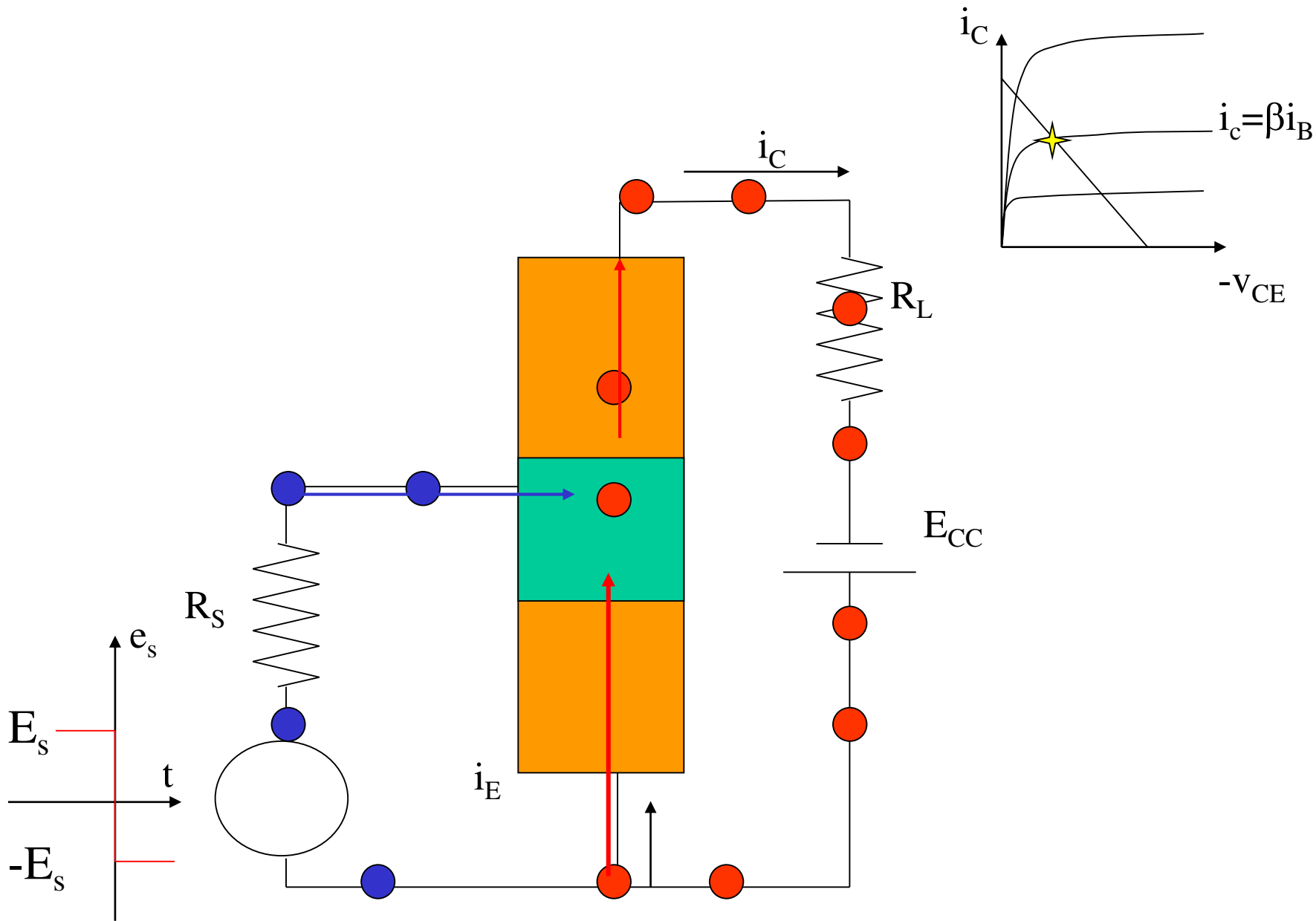

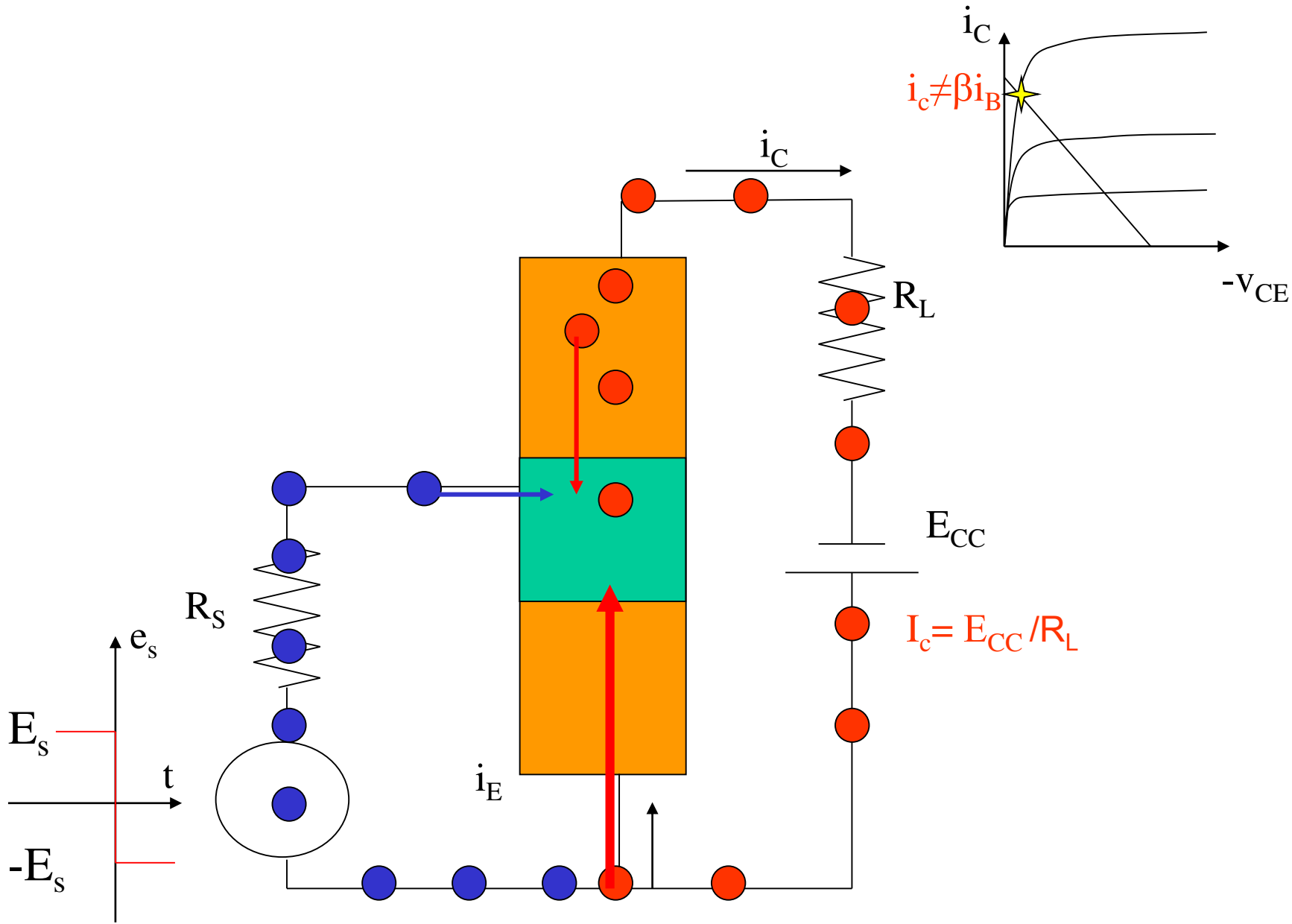


Switching cycle

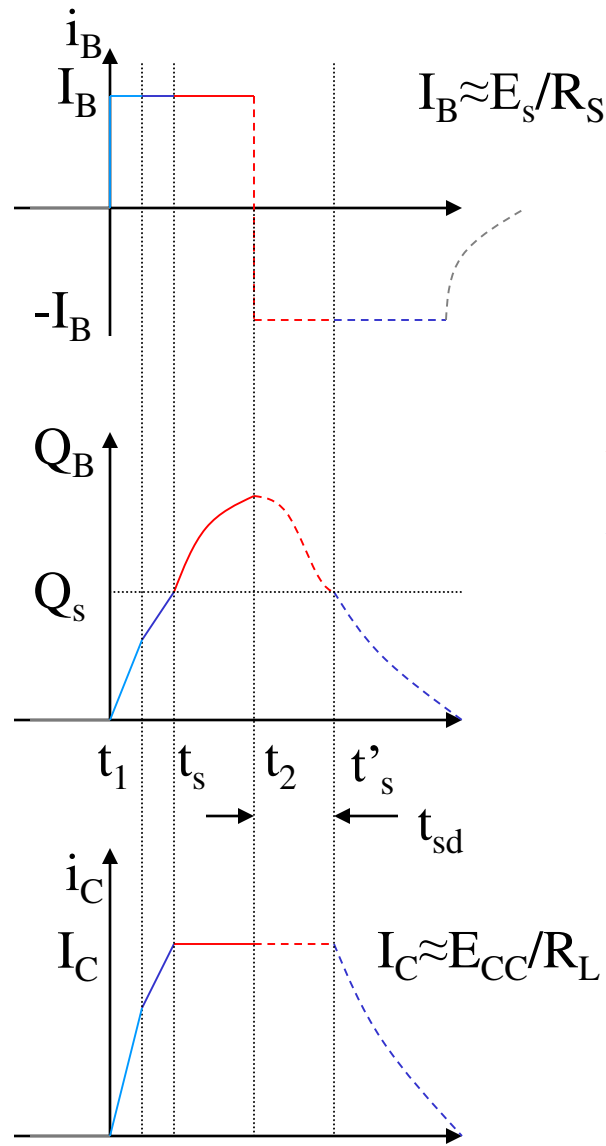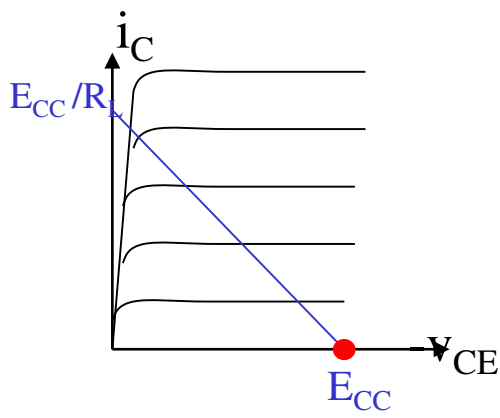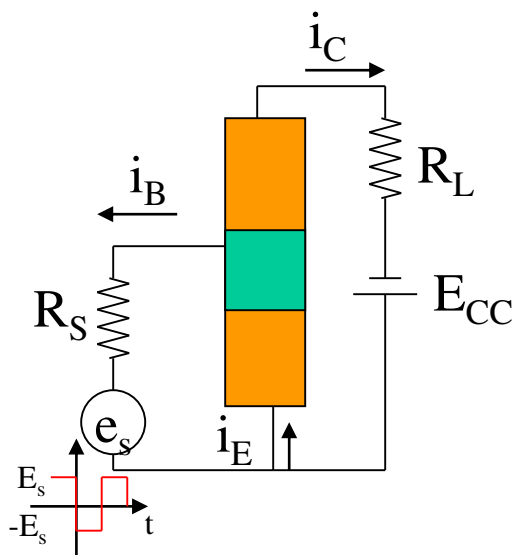

Switch to ON


Switch OFF

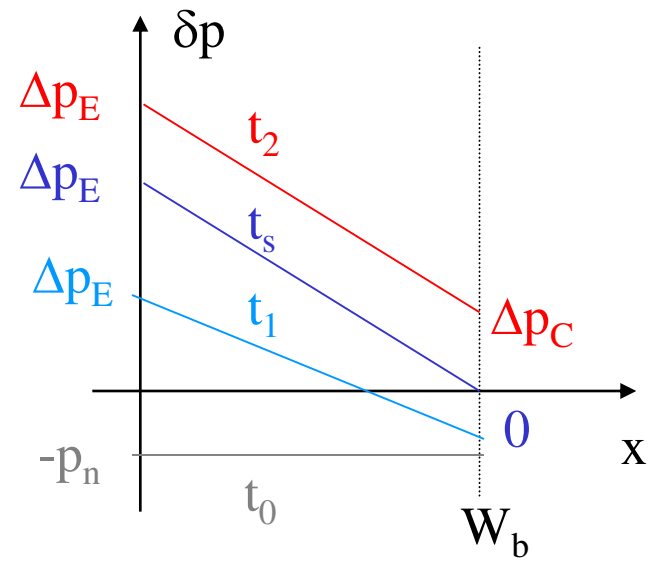

Charge in base (linear)


- Cut-off

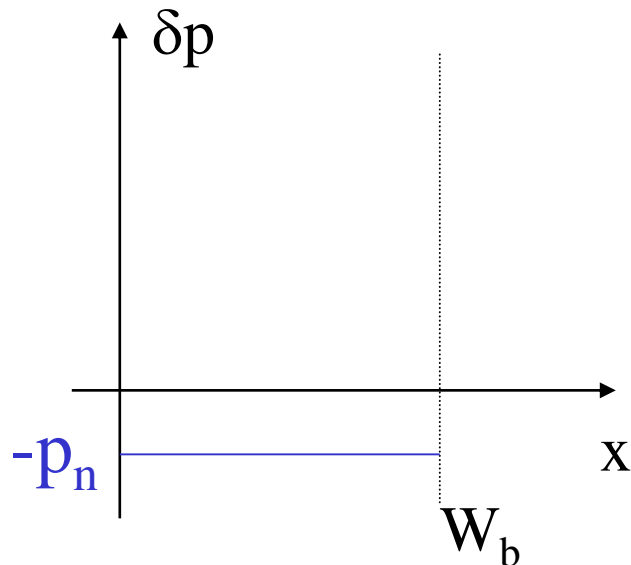- $V_{EB} < 0$ & $V_{BC} < 0$
- $\Delta p_E = -p_n$ & $\Delta p_C = -p_n$



- Saturation

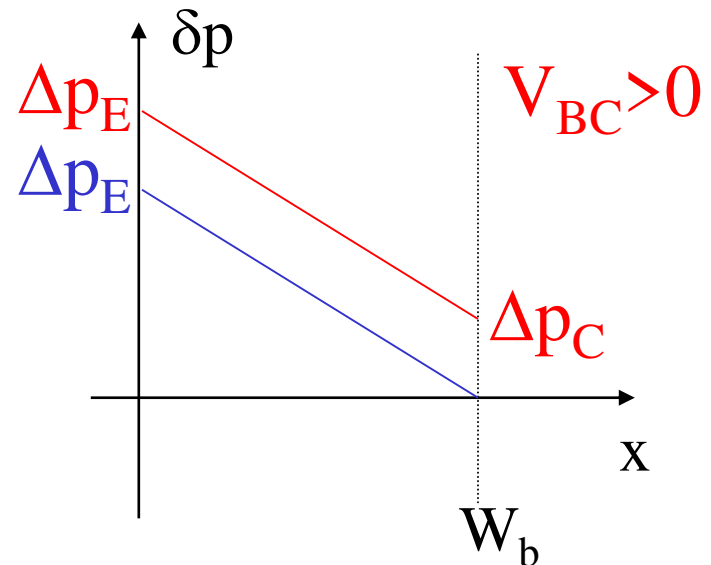- $V_{EB} > 0$ & $V_{BC} \geq 0$
- $\Delta p_E = p_n (e^{eV_{EB}/kT} - 1)$
- $\Delta p_C = 0$ ($V_{BC} = 0$)



Currents - review.

forward active mode

$$I_E = I_{pEB} + I_{nEB}$$


$$I_C = I_{pBC} + I_{nBC}$$

$$I_C \approx I_{pBC}$$

$$I_E = I_B + I_C$$



$$I_B = I_E - I_C$$
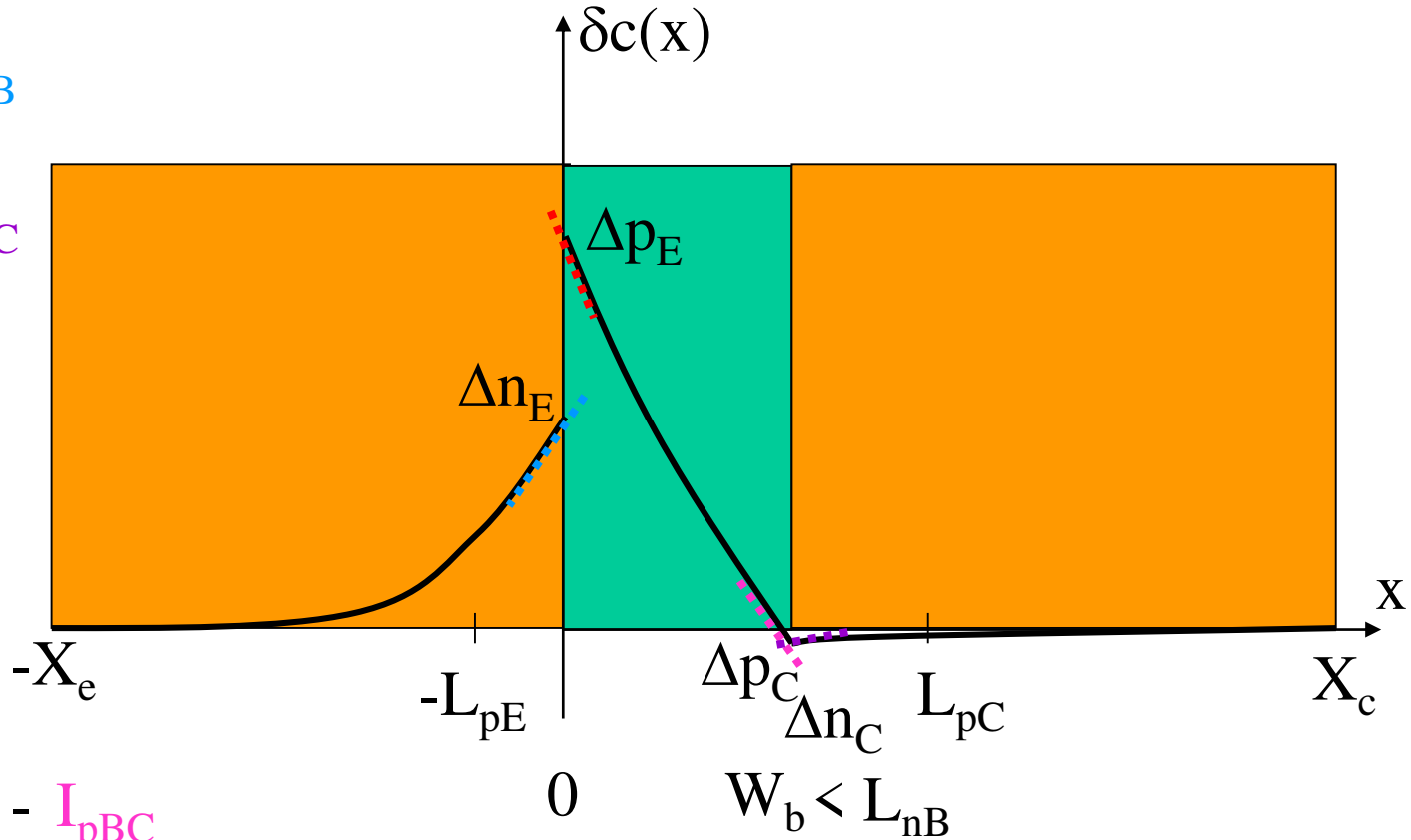
$$I_B = I_{nEB} + \underbrace{I_{pEB} - I_{pBC}}_{\text{Term due to recombination}}$$




Switching cycle - review



Common emitter circuit

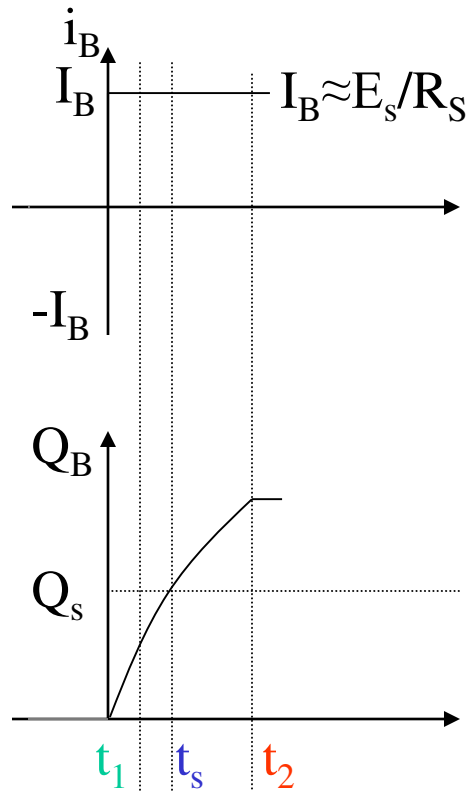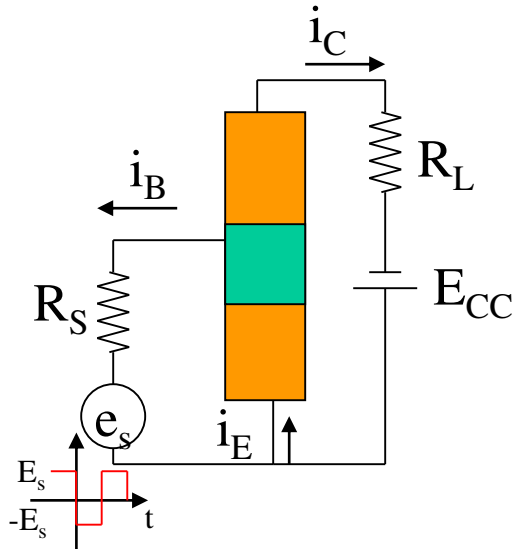

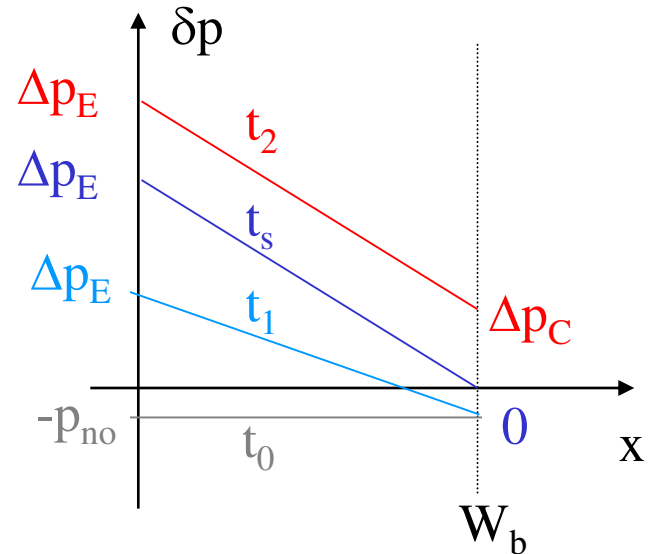Switch to ON
 With $I_B > I_C^{\max}/\beta$
 Over-saturation




Load line technique

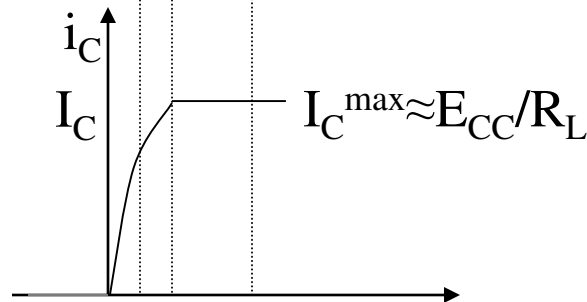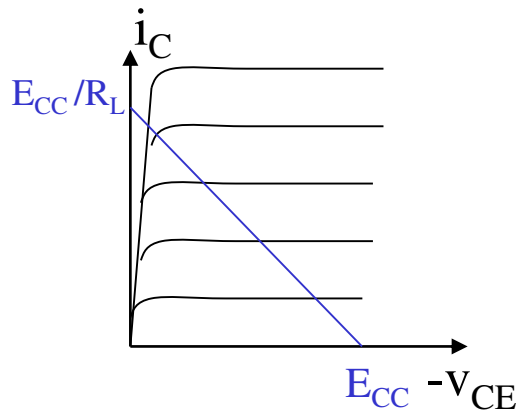



$$p_{no} \ll \Delta p_E$$

Switching cycle - review


Common emitter circuit

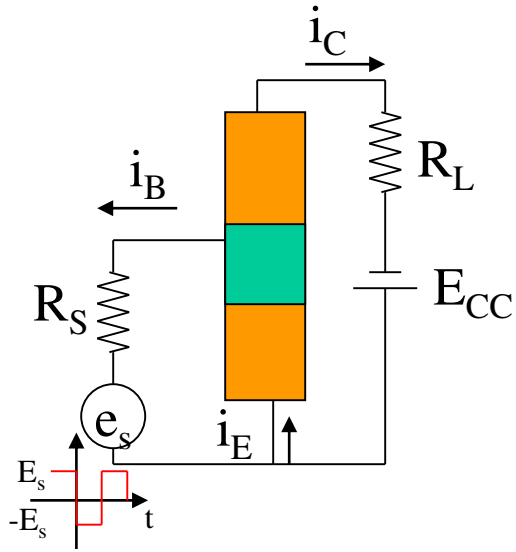





Load line technique

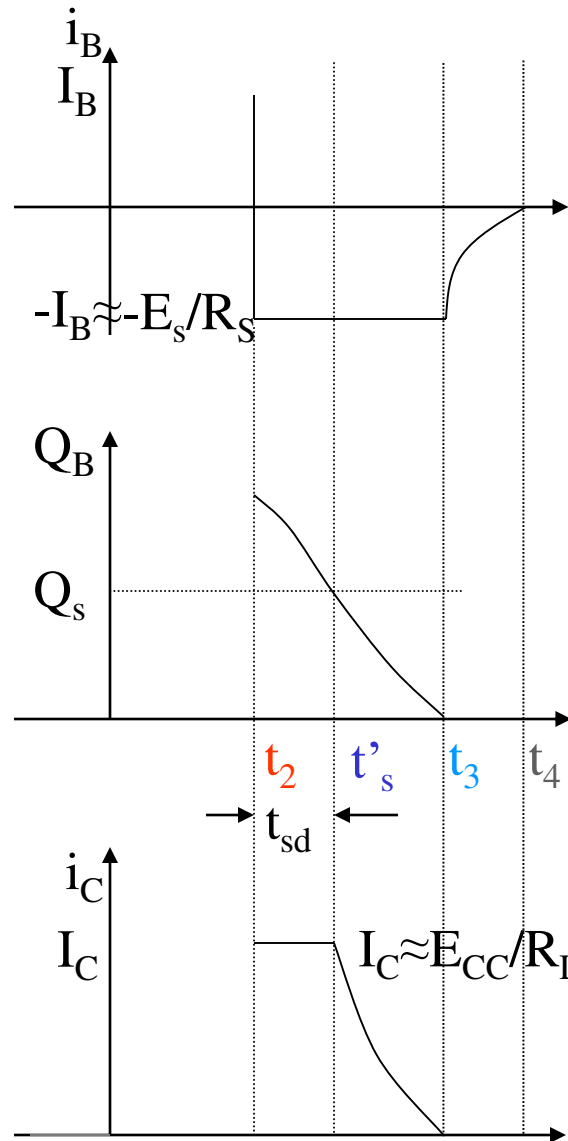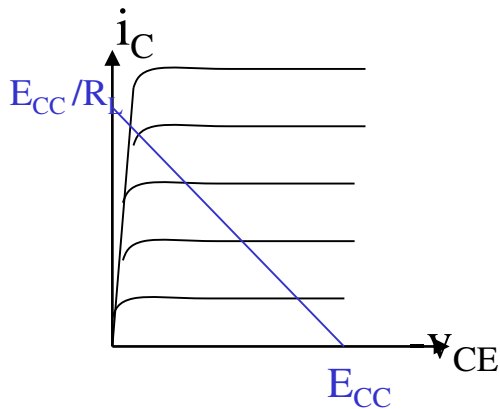


Switch OFF

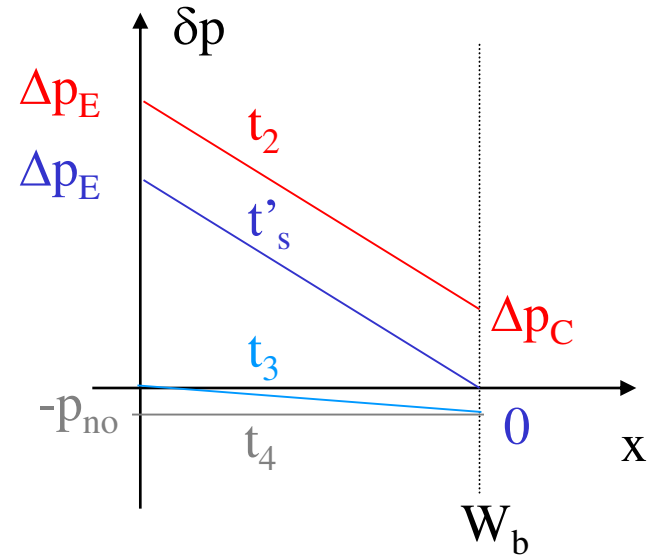

ON switching OFF=0→ON

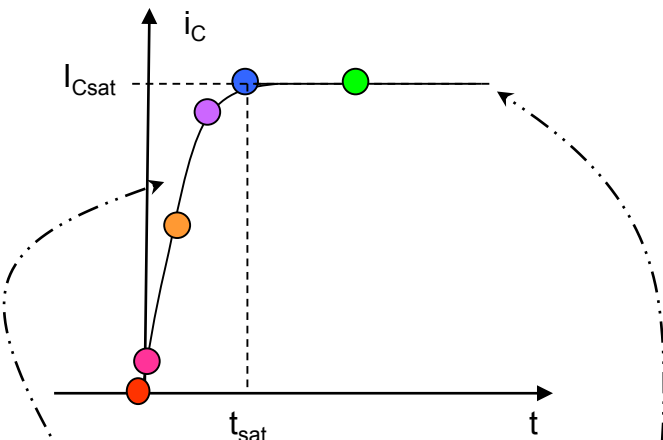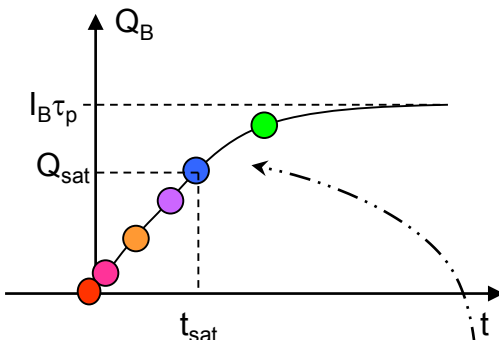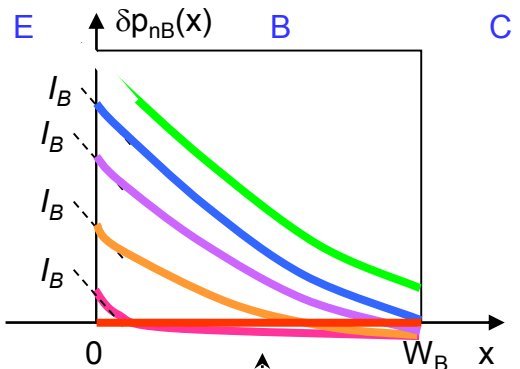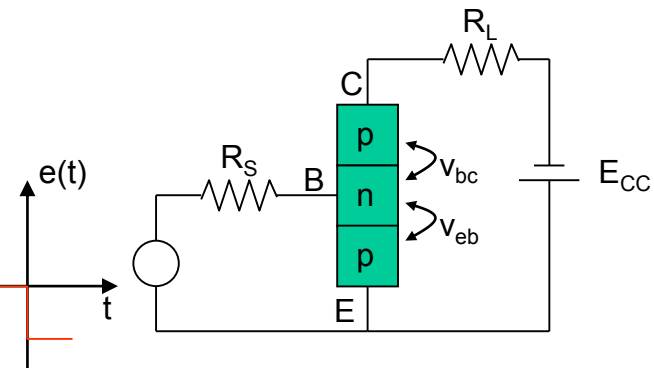

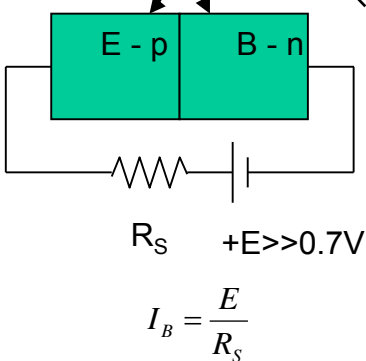$t < 0$
 $t \geq 0$
 $v_{eb} = 0 \rightarrow \text{ON} \approx 0.7V$



$$i(t) = \frac{dQ_B(t)}{dt} + \frac{Q_B(t)}{\tau_p}$$

$$\Rightarrow Q_B = I_B \tau_p \left[1 - \exp\left(\frac{-t}{\tau_p}\right) \right]$$

&

$$Q_B = \int_{x=0}^{x=W_B} e A \delta n_{pB}(x) dx$$

$$t < t_{sat} \quad i_C(t) = \frac{Q_B(t)}{\tau_t} = \frac{I_B \tau_p}{\tau_t} \left[1 - \exp\left(\frac{-t}{\tau_p}\right) \right]$$



$t \geq t_{sat}$

$$i_C(t) = \frac{E_{CC}}{R_L} = I_{Csat}$$

Driving off






Time to turn the BJT OFF is determined by:

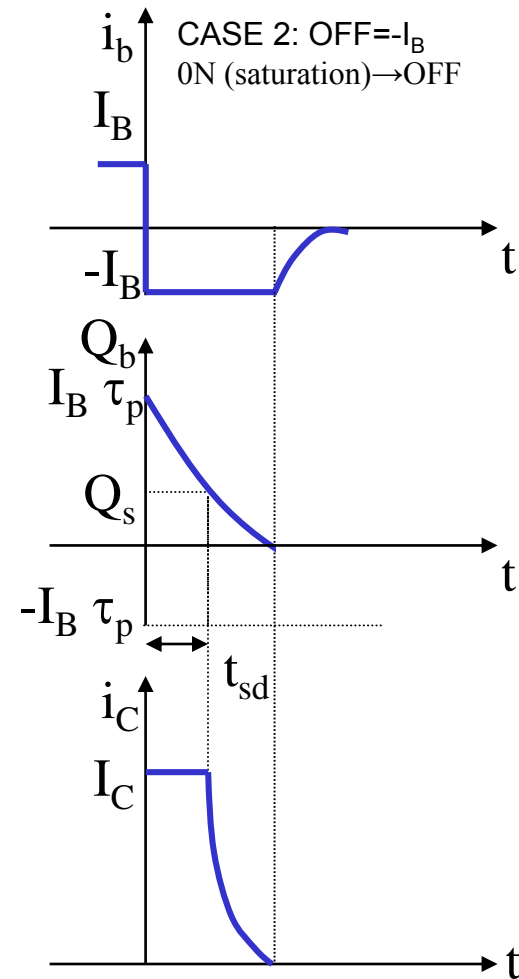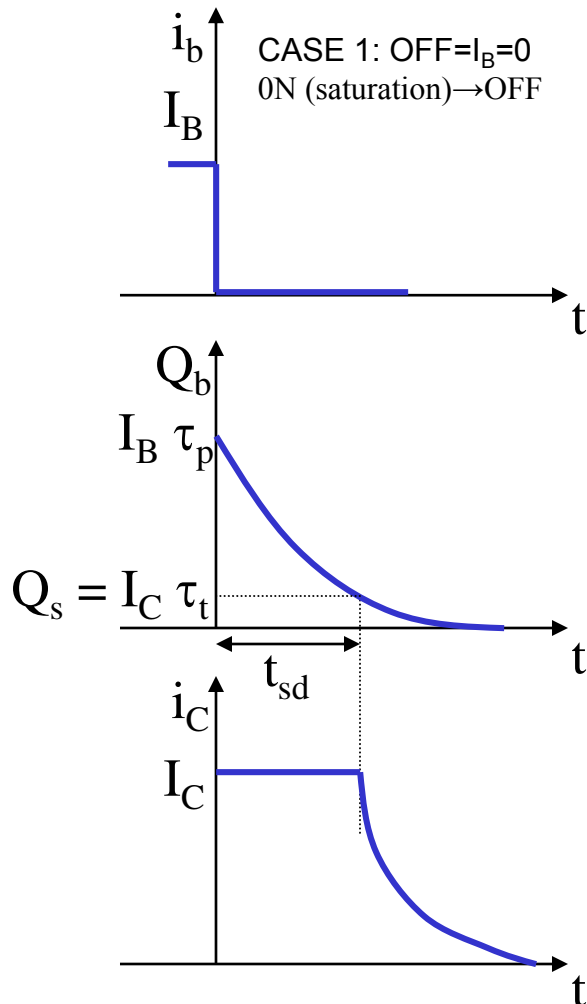- 1) The degree of over-saturation (BC junction)
- 2) The off-switching of the emitter-base diode



OFF switching

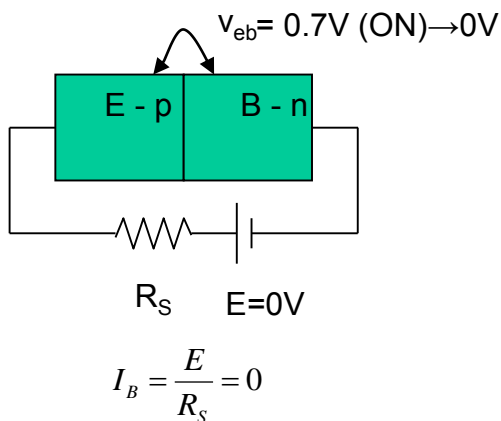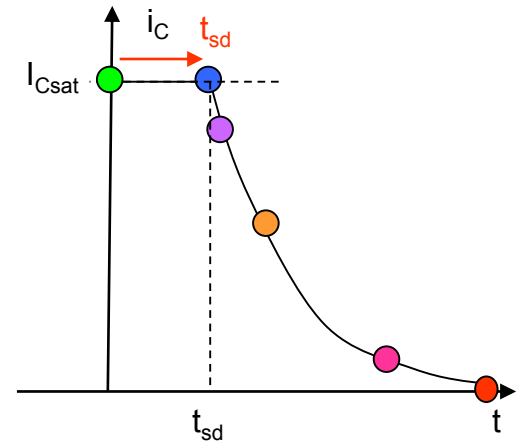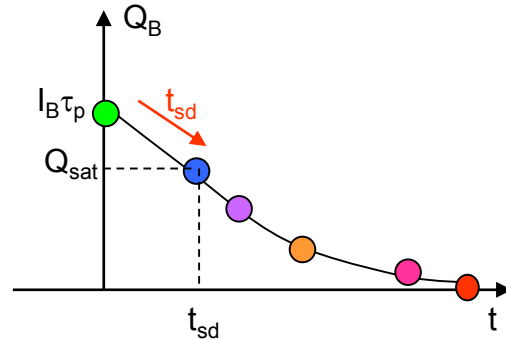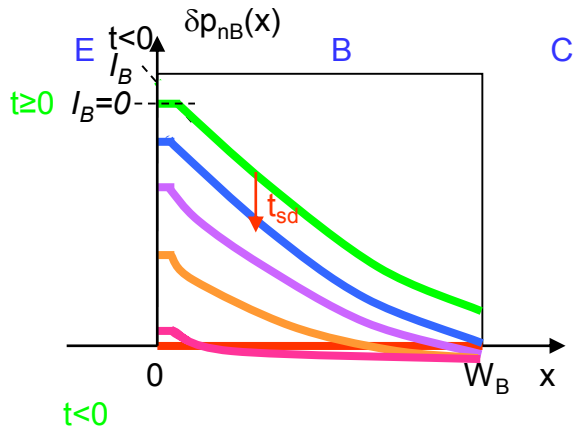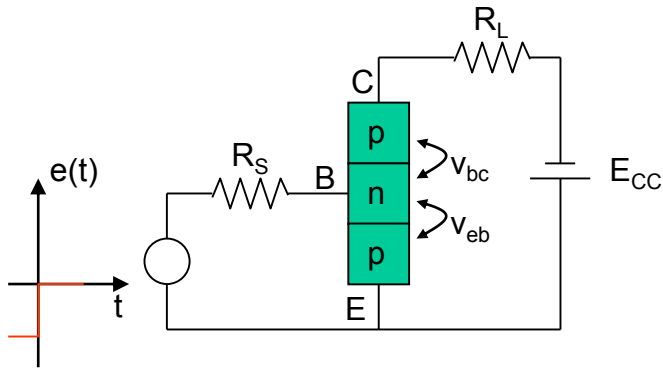ON (saturation) → OFF - CASE 1: OFF = $I_B = 0$



$$i(t) = \frac{dQ_B(t)}{dt} + \frac{Q_B(t)}{\tau_p}$$

⇒

$$Q_B(t) = I_B \tau_p \exp\left(\frac{-t}{\tau_p}\right)$$

&

$$Q_B = \int_{x=0}^{x=W_B} e A \delta n_{pB}(x) dx$$






$t < t_{sd}$

$$i_C(t) = \frac{E_{CC}}{R_L} = I_{Csat}$$

$t \geq t_{sd}$

$$i_C(t) = \frac{Q_B(t)}{\tau_t} = \frac{I_B \tau_p}{\tau_t} \exp\left(\frac{-t}{\tau_p}\right)$$

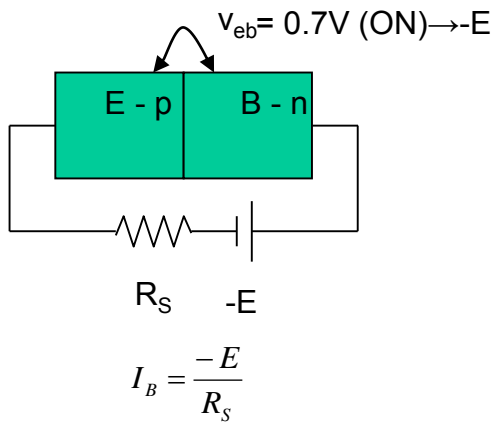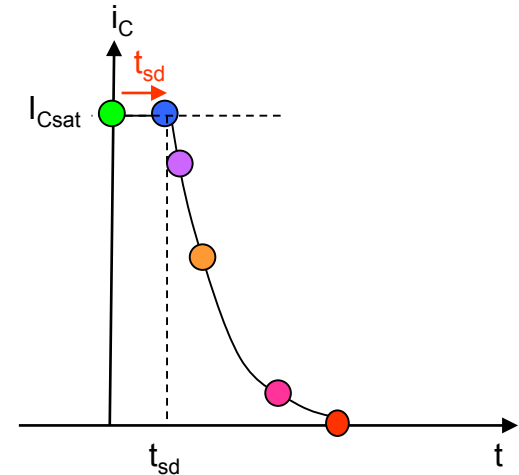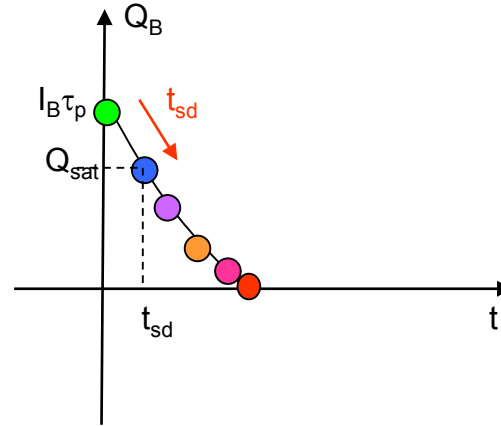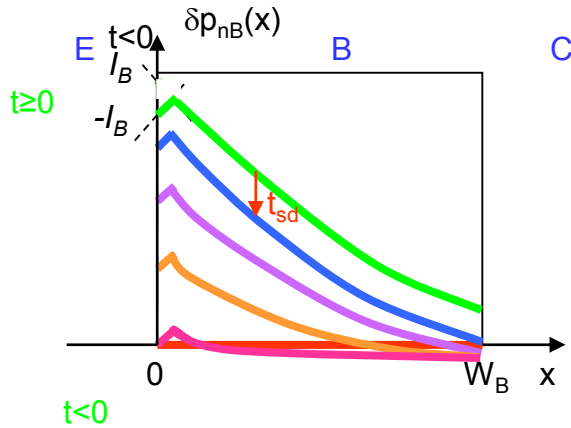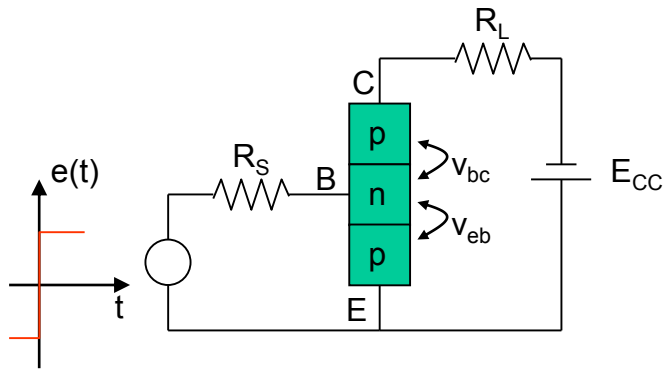ON (saturation) → OFF - CASE 2: OFF = -I_B



$$i(t) = \frac{dQ_B(t)}{dt} + \frac{Q_B(t)}{\tau_p}$$

⇒

$$Q_B(t) = I_B \tau_p \left[2 \exp\left(\frac{-t}{\tau_p}\right) - 1 \right]$$

&

$$Q_B = \int_{x=0}^{x=W_B} e A \delta n_{pB}(x) dx$$


$t < t_{sd}$

$$i_C(t) = \frac{E_{CC}}{R_L} = I_{Csat}$$


$t \geq t_{sd}$

$$i_C(t) = \frac{Q_B(t)}{\tau_t} = \frac{I_B \tau_p}{\tau_t} \left[2 \exp\left(\frac{-t}{\tau_p}\right) - 1 \right]$$

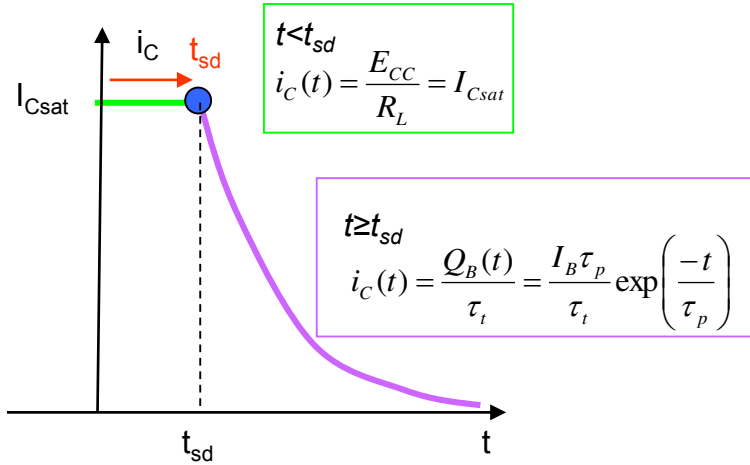ON (saturation) → OFF - CASE 1: OFF = $I_B = 0$



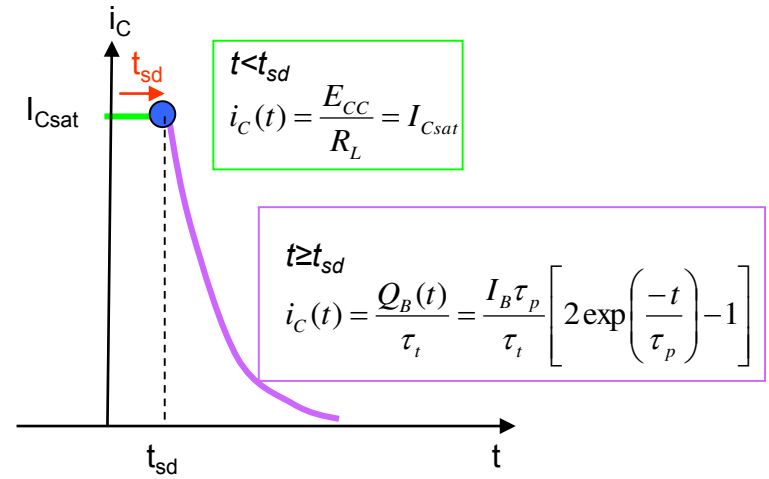
ON (saturation) → OFF - CASE 1: OFF = $-I_B$



STORAGE DELAY TIME: t_{sd} ●

$$i_C(t_{sd}) = I_{Csat} = \frac{E_{CC}}{R_L} = \frac{I_B \tau_p}{\tau_t} \exp\left(\frac{-t_{sd}}{\tau_p}\right)$$

 
$$i_C(t_{sd}) = I_{Csat} = \frac{E_{CC}}{R_L} = \frac{I_B \tau_p}{\tau_t} \left[2 \exp\left(\frac{-t_{sd}}{\tau_p}\right) - 1 \right]$$



shorter delay



Transients

Turn-on: off to saturation

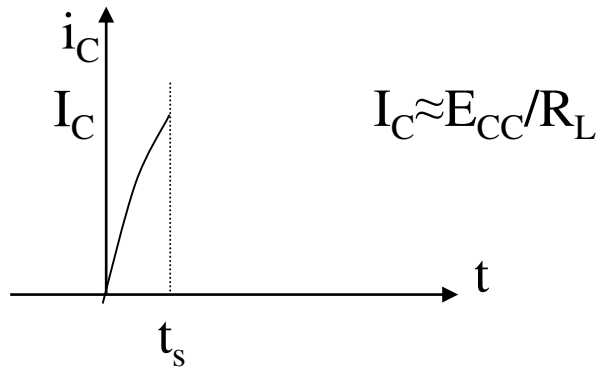


Time to saturation

ON switching OFF=0 → ON

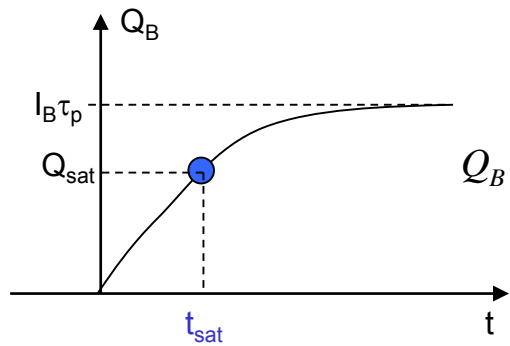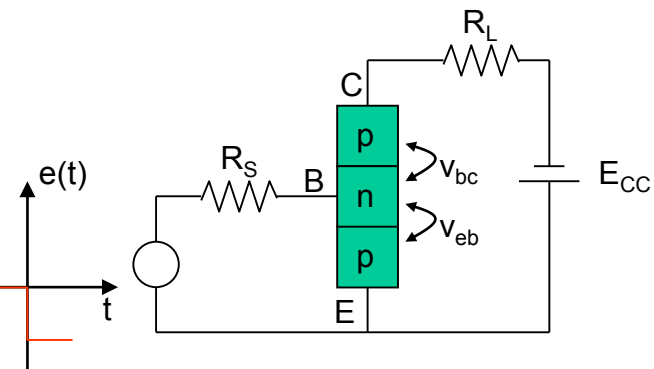
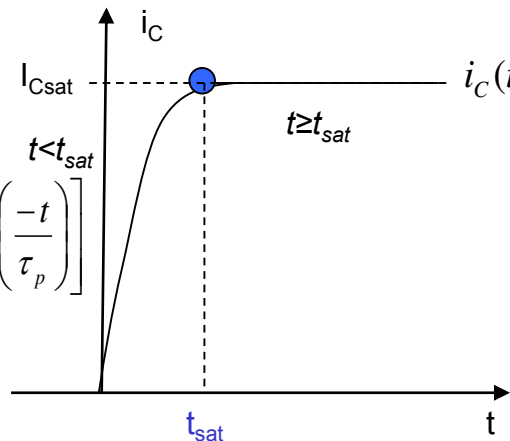
$$Q_B = I_B \tau_p \left[1 - \exp\left(\frac{-t}{\tau_p}\right) \right]$$



$$i_C(t) = \frac{E_{CC}}{R_L} = I_{Csat}$$

$$i_C(t) = \frac{Q_B(t)}{\tau_t} = \frac{I_B \tau_p}{\tau_t} \left[1 - \exp\left(\frac{-t}{\tau_p}\right) \right]$$

$$t = t_{sat} \quad i_C(t_{sat}) = \frac{I_B \tau_p}{\tau_t} \left[1 - \exp\left(\frac{-t_{sat}}{\tau_p}\right) \right] = I_{Csat}$$